



ABU DHABI UNIVERSITY

CEN - 466 ADVANCED DIGITAL DESIGN

Lab Report 3

Sequential Circuits: FSMs

Author:

Muhammad Obaidullah 1030313
Mohammed Farooq 1007778
Mehdi Ismail 1005689

Supervisor:

Dr. Mohammed Assad Ghazal

Section 1

December 8, 2012

Abstract

In this lab we were taught how to use VHDL to solve any problem using Finite State Machine method. Finite state machine is sequential type of implementation. In this Lab we wrote a simple FSM code to jump from one state to another by the use of Clock.

1 Introduction

Some times some problems cannot be simplified to be solved easily by using the traditional combinational logic. Therefore, we use another approach to the method and that is using the clock we break down the problem into sequences of steps / instructions / commands. These instructions are followed in a particular sequence depending upon the clock signal given to them as counter of program execution progress.

Finite State machine method involves solving a problem by thinking of the problem from the view point of a bunch of inputs, outputs and states. In this way we can solve any type of problem regardless of its difficulty. In this lab we tried to make VHDL standard FSM code for these kinds of problems.

2 Experiment Set-up

The Experiment was set up by opening and setting up the VHDL coding Integrated Development Environment Quartus II. The code was written in the Quartus IDE and then we debugged it. After debugging, We assigned the outputs to the pins on the ALTERA board. These outputs can be anything ranging from LEDs to Buzzers. Additionally, there were some inputs to be assigned to or how else could we get the input from the user. These all pins were assigned by referring to the Datasheet of the ALTERA Cyclone II and were assigned by the Pin Planner inside the Quartus.

3 List of Equipment used

- Power cable for Altera board.
- USB cable.
- A PC running Quartus II.
- Altera board.

4 Procedure

- Open Quartus.
- Click on Create a new project.
- Click next.
- Create a folder on a directory of your choice and select it as a working directory for you project.
- Name your project and click next.

- Now choose the board to be “EP2C35F672C6”.
- Click next and finish.
- Now go to File > New > VHDL File.
- Start writing the code.

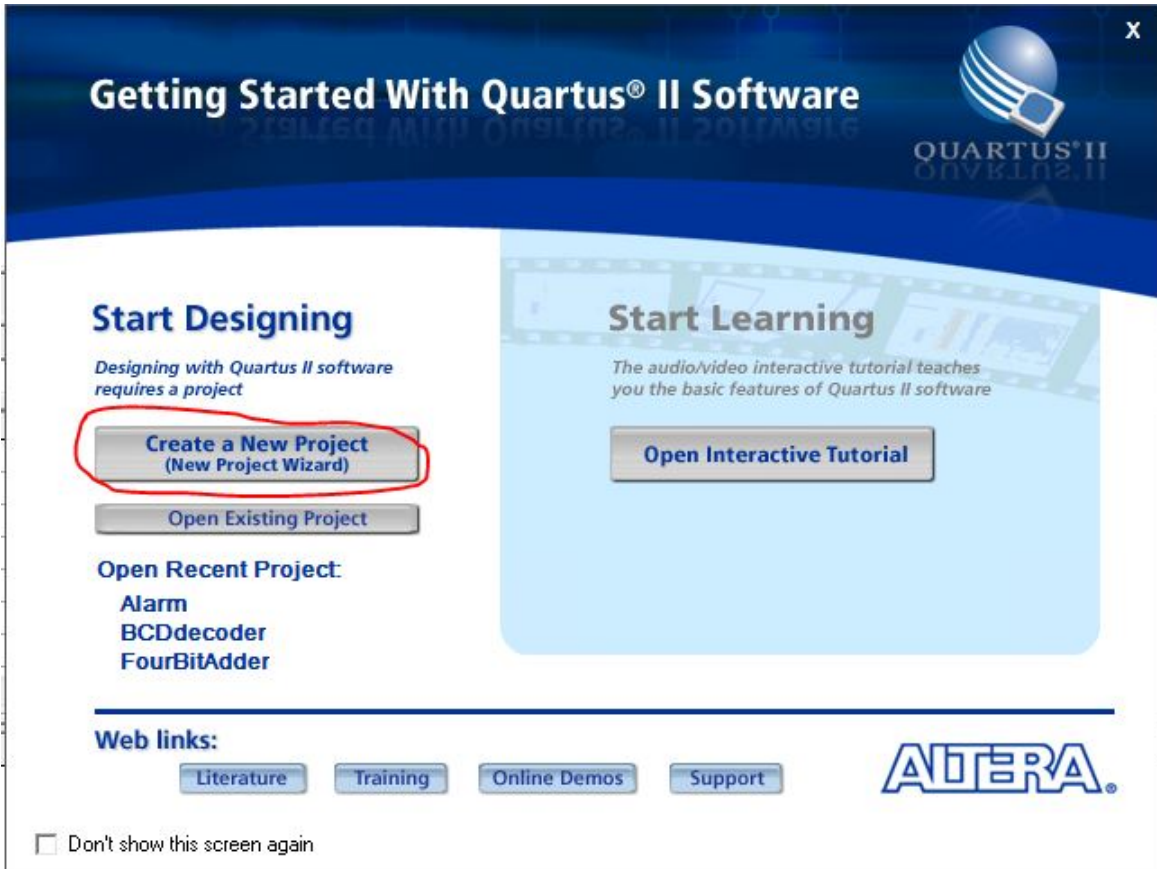


Figure 1: Click on “Create a New Project”.

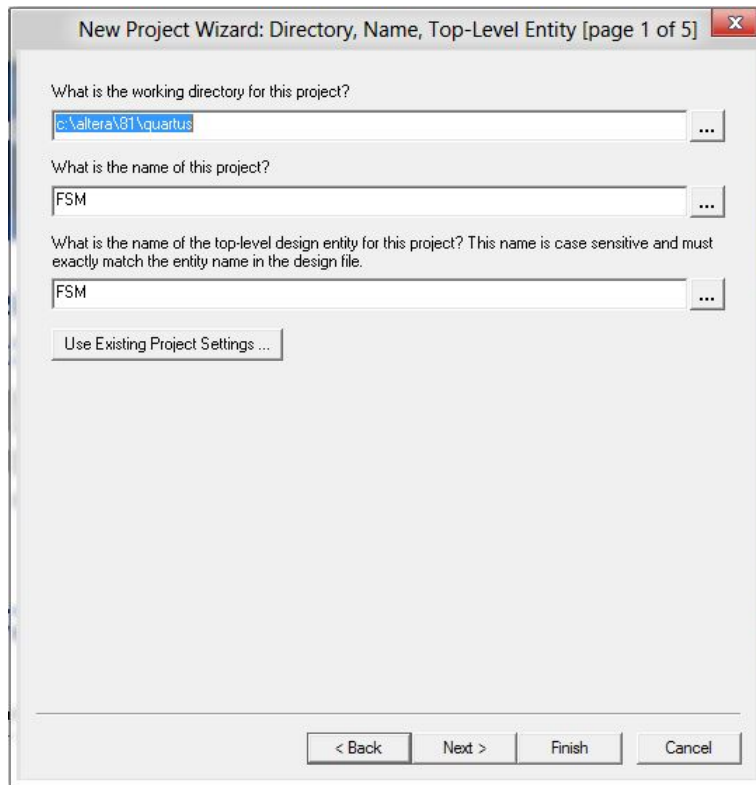


Figure 2: Choose the directory and name it without spaces and special characters.

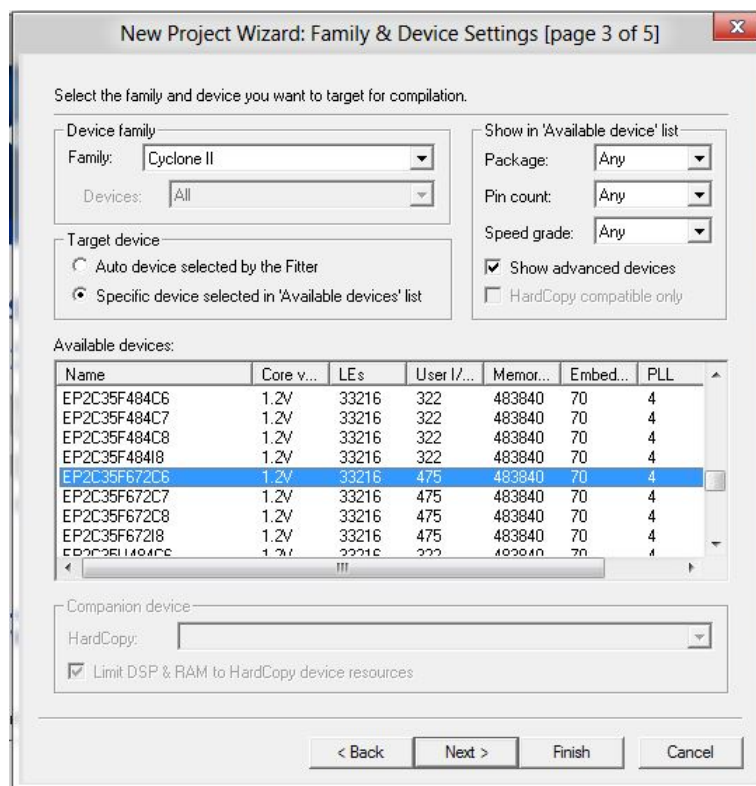


Figure 3: Choose the highlighted board and the Family should be “Cyclone II”.

5 Main Entity “FSM” Code

```
1  -- Basic libraries to include --
   library ieee ;
3  use ieee.std_logic_1164.all;

5  -- The main Entity --
   entity FSM is
7  port( n:    in std_logic;
        clock: in std_logic;
9         reset: in std_logic;
        y:    out std_logic_vector(3 downto 0)
11 );
   end FSM;

13
   -- The architecture of FSM Entity --
15 architecture FSM_arch of FSM is
   component clk_div IS
17 PORT( clock_50Mhz : IN STD_LOGIC; -- The input to the clock divider is from the pin
        assignment and takes 50 MHz input
        clock_1MHz : OUT STD_LOGIC; -- 50 MHz divided to give 1 MHz Output
19        clock_100KHz : OUT STD_LOGIC; -- 50 MHz divided to give 100 KHz Output
        clock_10KHz : OUT STD_LOGIC; -- 50 MHz divided to give 10 KHz Output
21        clock_1KHz : OUT STD_LOGIC; -- 50 MHz divided to give 1 KHz Output
        clock_100Hz : OUT STD_LOGIC; -- 50 MHz divided to give 100 Hz Output
23        clock_10Hz : OUT STD_LOGIC; -- 50 MHz divided to give 10 Hz Output
        clock_1Hz : OUT STD_LOGIC); -- 50 MHz divided to give 1 Hz Output, which is
        basically one cycle per second.
25 END component;
        type state_type is (idle , washing , soaping , cleaning , drying); --Declaring all
        the 5 states
27        signal next_state , current: state_type; --Declaring two wires to store the
        current and the next state
        signal clk1hz: std_logic;
29 begin
        gate1: clk_div port map (clock_50Mhz=>clock , clock_1Hz=>clk1hz); -- Taking the 1Hz
        output so that every one second the state is changed
31        state_reg: process(clk1hz , reset)
        begin
33        if (reset='1') then -- If Reset is one, then go immediately to Idle State
                current <= idle;
35        elsif (clk1hz'event and clk1hz='1') then
                current <= next_state;
37        end if;
        end process;
39        state_machine: process(current , n)
        begin
41
43        case current is
        when idle => y <= "0000"; -- All outputs are OFF in Idle State
        if n='0' then
45                next_state <= idle;
        elsif n='1' then
47                next_state <= washing;
        end if;
49        when washing => y <= "1000"; --First LED Lights up to show that it is in the
        Washing State
        if n='0' then
```

```

51     next_state<=washing;
    elsif n='1' then
53         next_state <= soaping;
    end if;
55     when soaping => y <= "0100"; --Second LED Lights up to show that it is in the
        Soaping State
    if n='0' then
57         next_state <= soaping;
    elsif n='1' then
59         next_state <= cleaning;
    end if;
61     when cleaning => y <= "0010"; --Third LED Lights up to show that it is in the
        Cleaning State
    if n='0' then
63         next_state <= cleaning;
    elsif n='1' then
65         next_state <= drying;
    end if;
67
    when drying => y <= "0001"; --Fourth LED Lights up to show that it is in the
        Drying State
69     if n='0' then
        next_state <= drying;
71     elsif n='1' then
        next_state <= idle; --Go Back to Idle state Again
73     end if;
        when others =>
75         y <= "0000";
        next_state <= idle;
77     end case;
    end process;
79 end FSM_arch;

```

6 Entity “CLKDIV” Code

```

1  LIBRARY IEEE;
   USE IEEE.STD_LOGIC_1164.all;
3  USE IEEE.STD_LOGIC_ARITH.all;
   USE IEEE.STD_LOGIC_UNSIGNED.all;
5  ENTITY clk_div IS
   PORT( clock_50Mhz : IN STD_LOGIC;
7     clock_1MHz : OUT STD_LOGIC;
        clock_100KHz : OUT STD_LOGIC;
9     clock_10KHz : OUT STD_LOGIC;
        clock_1KHz : OUT STD_LOGIC;
11    clock_100Hz : OUT STD_LOGIC;
        clock_10Hz : OUT STD_LOGIC;
13    clock_1Hz : OUT STD_LOGIC);
   END clk_div;
15 ARCHITECTURE Behavior OF clk_div IS
   SIGNAL count_1Mhz : STD_LOGIC_VECTOR(5 DOWNTO 0);
17   SIGNAL count_100Khz, count_10Khz, count_1Khz : STD_LOGIC_VECTOR(2 DOWNTO 0);
   SIGNAL count_100hz, count_10hz, count_1hz : STD_LOGIC_VECTOR(2 DOWNTO 0);
19   SIGNAL clock_1Mhz_int, clock_100Khz_int : STD_LOGIC;
   SIGNAL clock_10Khz_int, clock_1Khz_int : STD_LOGIC;

```

```

21 SIGNAL clock_100hz_int , clock_10Hz_int   : STD_LOGIC;
22 SIGNAL clock_1Hz_int       : STD_LOGIC;
23 BEGIN
24   PROCESS
25   BEGIN
26     -- Divide by 50
27     WAIT UNTIL clock_50Mhz 'EVENT and clock_50Mhz = '1';
28     IF count_1Mhz < 49 THEN
29       count_1Mhz <= count_1Mhz + 1;
30     ELSE
31       count_1Mhz <= "000000";
32     END IF;
33     IF count_1Mhz < 24 THEN
34       clock_1Mhz_int <= '0';
35     ELSE
36       clock_1Mhz_int <= '1';
37     END IF;
38     -- Ripple clocks are used in this code to save prescaler hardware
39     -- Sync all clock prescaler outputs back to master clock signal
40     clock_1Mhz   <= clock_1Mhz_int;
41     clock_100Khz <= clock_100Khz_int;
42     clock_10Khz  <= clock_10Khz_int;
43     clock_1Khz   <= clock_1Khz_int;
44     clock_100hz  <= clock_100hz_int;
45     clock_10hz   <= clock_10hz_int;
46     clock_1hz    <= clock_1hz_int;
47   END PROCESS;
48   -- Divide by 10
49   PROCESS
50   BEGIN
51     WAIT UNTIL clock_1Mhz_int 'EVENT and clock_1Mhz_int = '1';
52     IF count_100Khz /= 4 THEN
53       count_100Khz <= count_100Khz + 1;
54     ELSE
55       count_100Khz <= "000";
56       clock_100Khz_int <= NOT clock_100Khz_int;
57     END IF;
58   END PROCESS;
59   -- Divide by 10
60   PROCESS
61   BEGIN
62     WAIT UNTIL clock_100Khz_int 'EVENT and clock_100Khz_int = '1';
63     IF count_10Khz /= 4 THEN
64       count_10Khz <= count_10Khz + 1;
65     ELSE
66       count_10Khz <= "000";
67       clock_10Khz_int <= NOT clock_10Khz_int;
68     END IF;
69   END PROCESS;
70   -- Divide by 10
71   PROCESS
72   BEGIN
73     WAIT UNTIL clock_10Khz_int 'EVENT and clock_10Khz_int = '1';
74     IF count_1Khz /= 4 THEN
75       count_1Khz <= count_1Khz + 1;
76     ELSE
77       count_1Khz <= "000";
78       clock_1Khz_int <= NOT clock_1Khz_int;
79     END IF;

```

```

END PROCESS;
81 -- Divide by 10
PROCESS
83 BEGIN
    WAIT UNTIL clock_1Khz_int 'EVENT and clock_1Khz_int = '1';
85     IF count_100hz /= 4 THEN
        count_100hz <= count_100hz + 1;
87     ELSE
        count_100hz <= "000";
89     clock_100hz_int <= NOT clock_100hz_int;
        END IF;
91 END PROCESS;
-- Divide by 10
93 PROCESS
BEGIN
95     WAIT UNTIL clock_100hz_int 'EVENT and clock_100hz_int = '1';
        IF count_10hz /= 4 THEN
97         count_10hz <= count_10hz + 1;
        ELSE
99         count_10hz <= "000";
            clock_10hz_int <= NOT clock_10hz_int;
101        END IF;
    END PROCESS;
103 -- Divide by 10
PROCESS
105 BEGIN
    WAIT UNTIL clock_10hz_int 'EVENT and clock_10hz_int = '1';
107     IF count_1hz /= 4 THEN
        count_1hz <= count_1hz + 1;
109     ELSE
        count_1hz <= "000";
111     clock_1hz_int <= NOT clock_1hz_int;
        END IF;
113 END PROCESS;
END Behavior;

```

7 Results and Discussions

- After compiling the code successful uploading and running of the Altera Board was achieved.
- Whenever the clock button was pressed, the state was changed to the next one and the next two LEDs lit up.

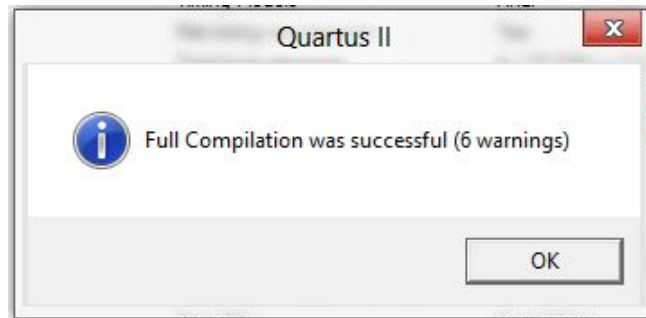


Figure 4: After writing the code, a successful compilation of the code was achieved.



Figure 5: LED for the first state is turned ON after 1 second.



Figure 6: LED for the second state is turned ON after 1 second

 


Figure 7: LED for the Third state is turned ON after 1 second.



Figure 8: LED for the Fourth state is turned ON after 1 second.



Figure 9: When the “RESET” button is pressed, the whole system comes to a halt and no LED is lit up as the system is in idle state where no LEDs should be ON.



Figure 10: When the “SET” button is switched ON, the system continues to work with normal functionality.

8 Conclusion

- This was just a basic FSM, and it can be changed later to add or subtract states and make it a more complex design.
- Solving a problem using FSM is much easier than doing it combinationally.
- FSM allows us to think of the outputs and inputs and build them into a number of stages.

9 Team Dynamics

Report/Member	Weight/Grade	Obaidullah	Farooq	Mehdi Ismail
Abstract	20%	65%	15%	15%
Introduction	10%	0%	50%	50%
Procedure Part 1	10%	100%	0%	0%
Procedure Part 2	10%	0%	100%	0%
Procedure Part 3	10%	0%	0%	100%
Results Part 1	10%	100%	0%	0%
Results Part 2	10%	0%	100%	0%
Results Part 3	10%	0%	0%	100%
Conclusion	10%	0%	50%	50%
Claimed Contribution		33%	33%	33%
Contribution Validation Penalty		0%	0%	0%
Overall Contribution		33%	33%	33%
Overall Grade with Quality	100%	100.0%	100.0%	100.0%