



ABU DHABI UNIVERSITY

ELECTRIC CIRCUITS

Design Project
Problem 7.89

Author:
Muhammad Obaidullah
1030313

Supervisor:
Dr. Montasir Qasymeh

Section 1

August 13, 2012

Abstract

The design project is to solve Problem 7.89 (page 281) of the text book. I solved the problem analytically and also using the MULTISIM.

1 Question

The voltage pulse shown in *Figure 1* is applied to the ideal integrating amplifier shown in *Figure 2*. Derive the numerical expressions for $v(t)$ when $v(0) = 0$ for the time intervals

- $t < 0$.
- $0 \leq t \leq 250$ ms.
- 250 ms $\leq t \leq 500$ ms.
- 500 ms $\leq t < \infty$.

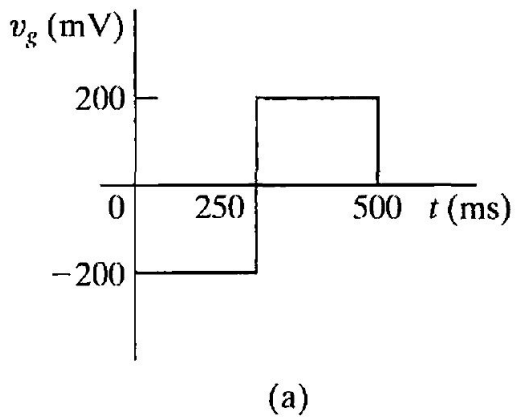


Figure 1: Voltage Pulse


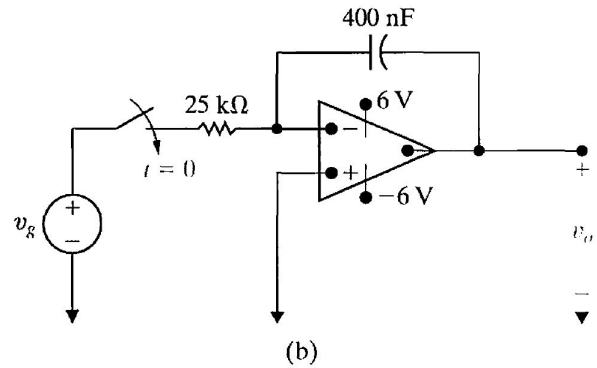


Figure 2: Integrating Amplifier

2 Answer

When switch is closed

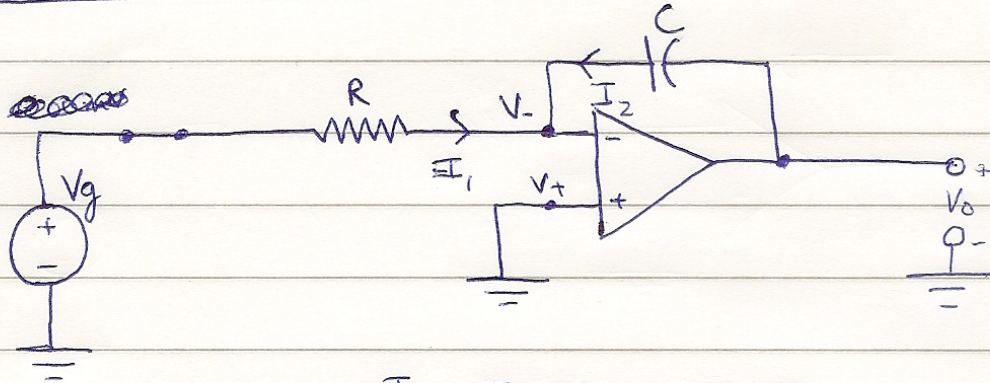

$$I_1 + I_2 = 0 \rightarrow (1)$$

$$\because V_- = V_+ = 0$$

$$I_1 = \frac{V_g}{R} \rightarrow (2)$$

$$I_2 = C \frac{dV_o}{dt} \rightarrow (3)$$

By (2) & (3) & (1)

we get
$$\frac{V_g}{R} + C \frac{dV_o}{dt} = 0$$

$$C \frac{dV_o}{dt} = - \frac{V_g}{R}$$

$$\frac{dV_o}{dt} = - \frac{V_g}{RC}$$

$$dV_o = - \frac{V_g}{RC} dt$$

$$\int_0^t dV_o = - \frac{1}{RC} \int_0^t V_g dt$$

$$V_o = - \frac{1}{RC} \int_0^t V_g dt$$

a) Switch is open, therefore no current is passing through V_- terminal and also $V_+ = 0V = V_-$ so V_o at any time $< 0s$ is $V_o = 0$.

b) $0 \leq t \leq 250ms$

$V_g = -200mV$ in this interval

Using formula on previous page

$$V_o = -\frac{1}{25 \times 10^3 \times 400 \times 10^{-9}} \int_0^t -200 \times 10^{-3} dt$$

$$\therefore \boxed{V_o = +100 \int_0^t +200 \times 10^{-3} dt}$$

↖ for any time between 0 and 250ms

c) $250ms \leq t \leq 500ms$

$V_g = +200mV$ for this interval

At $t = 250ms$ what is V_o ?

$$V_o = +100 (200 \times 10^{-3} \times 250 \times 10^{-3})$$

$$\boxed{V_o = 5V} \text{ at } 250ms$$

Applying formula

$$V_o = -100 \int_0^t V_g dt$$

$$V_o = -100 \int_{t_0}^t V_g dy + V_o(t_0)$$

$$\therefore \boxed{V_o = -100 \int_{250 \times 10^{-3}}^t 200 \times 10^3 dy + 5}$$

d) $500 \text{ ms} \leq t < \infty$

$V_g = 0 \text{ mV}$ for this interval

At time = 500 ms what was V_o ?

$$V_o = -100 \int_{250 \times 10^{-3}}^{500 \times 10^{-3}} 200 \times 10^{-3} dy + 5$$

$$V_o = -100 (200 \times 10^{-3} (500 \times 10^{-3} - 250 \times 10^{-3})) + 5$$

$$V_o = -100 (0.05) + 5$$

$$V_o = -5 + 5$$

$$V_o = 0$$

$$V_o \text{ at } 500 \text{ ms} = 0 \text{ V}$$

Applying formula

$$\therefore V_o = -100 \int_{500 \times 10^{-3}}^t 0 + 0$$

$\boxed{V_o = 0}$ for any time between ∞ and 500 ms

This is true because capacitor has fully discharged.

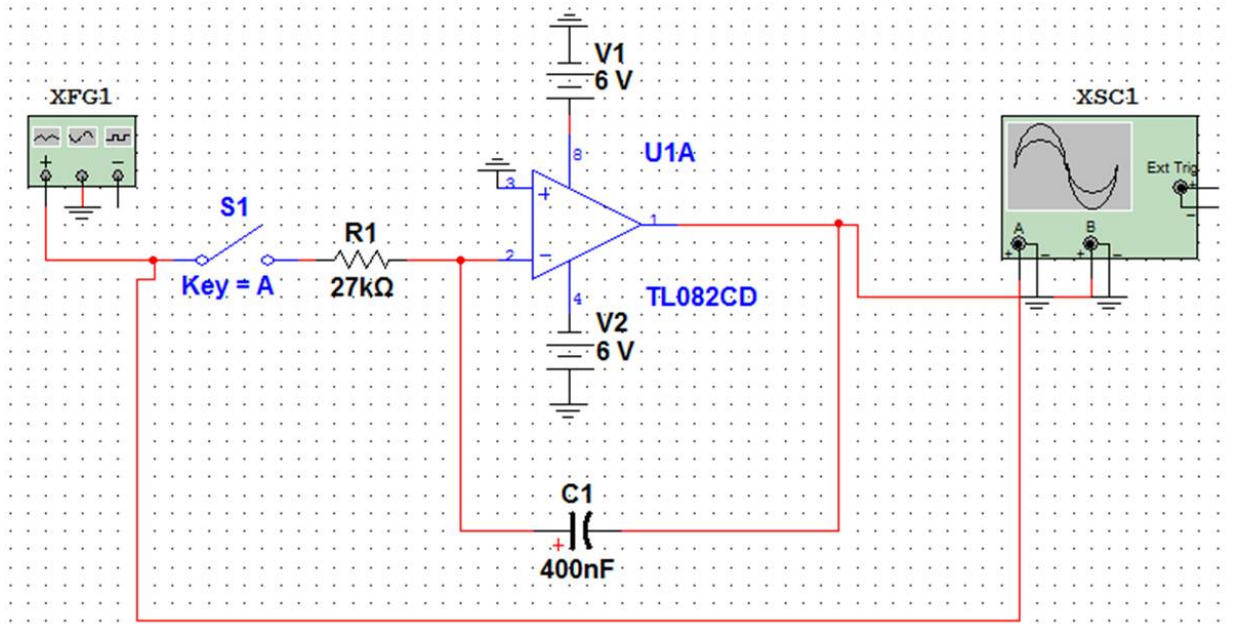


Figure 3: The following circuit was drawn and simulated in Multisim XFG1 is the function generator set according to figure 4. XSC1 is an oscilloscope to compare input and output signals

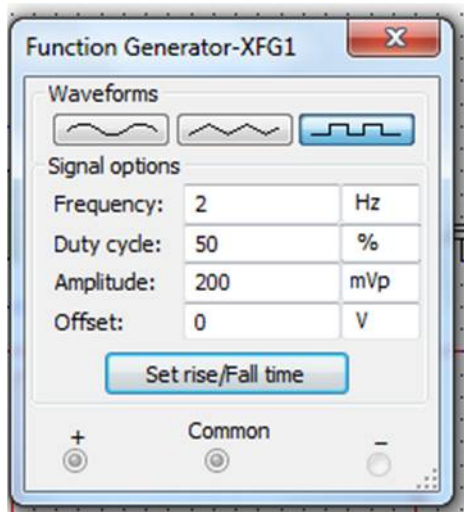


Figure 4: The Frequency Generator producing square wave of these features was provided as V_g to Negative input of Amplifier

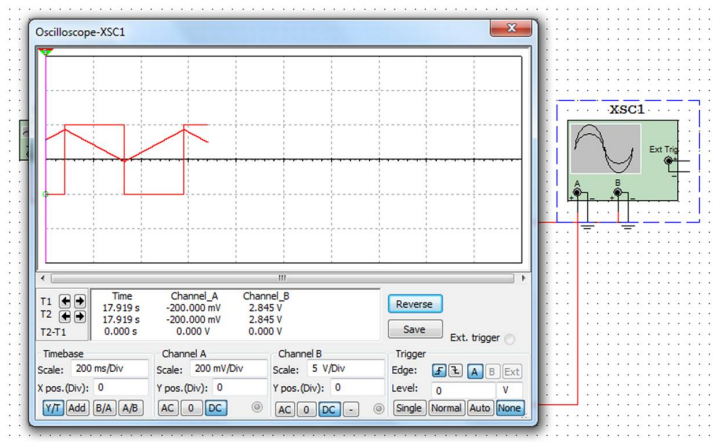


Figure 5: Seeing input V_g from Channel A and output V_o from Channel B

Detailed Analysis of the input voltage V_g and output voltage V_o showed that my equations resulted in close approximations

For Example:

V_o at time $t = 0$ ms is Approximately 0 V.

V_o at time $t = 250$ ms is Approximately 5 V.

V_o at time $t = 500$ ms is Approximately 0 V.

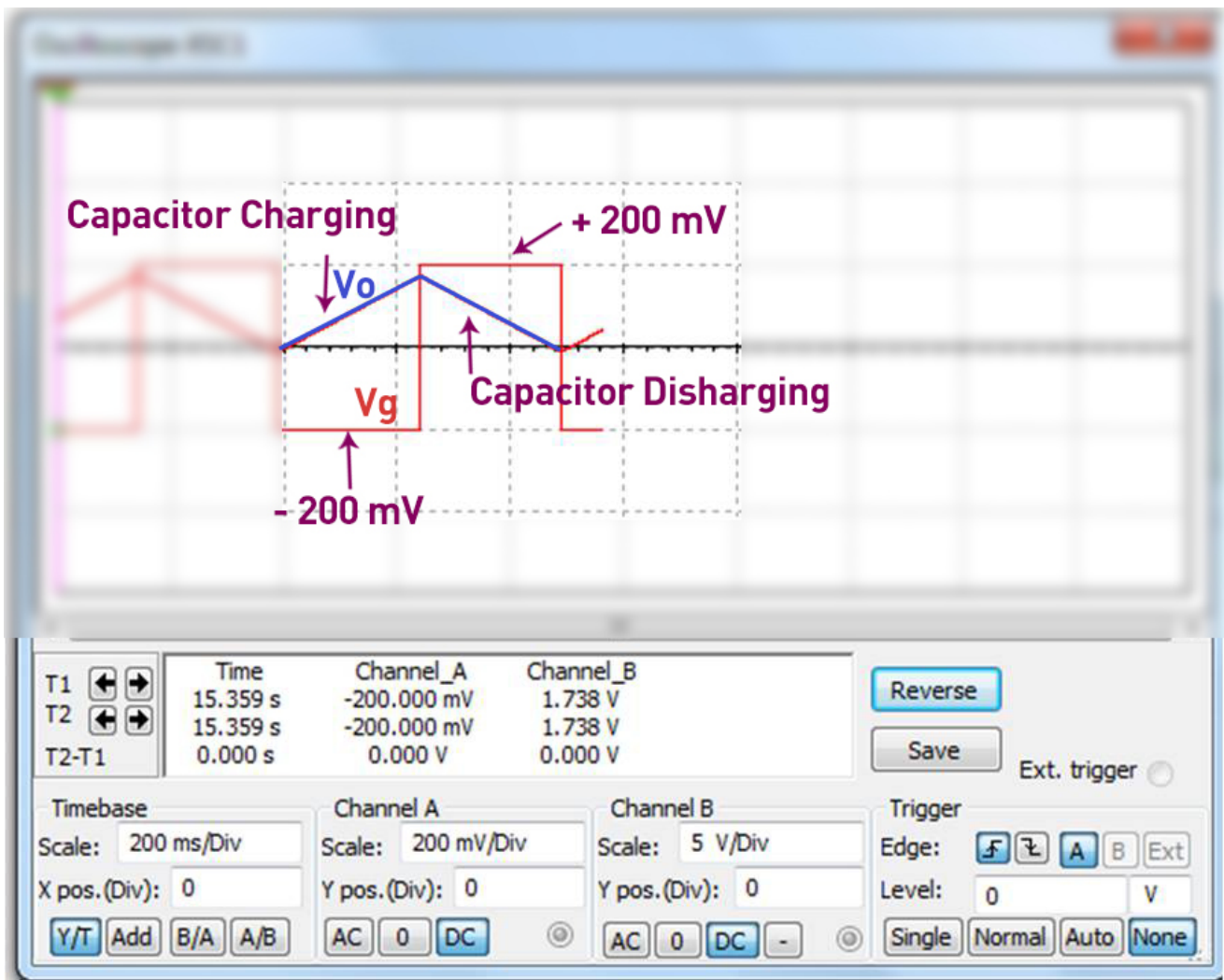


Figure 6: Detailed Explanation of the results using one portion of the signal at input V_g