
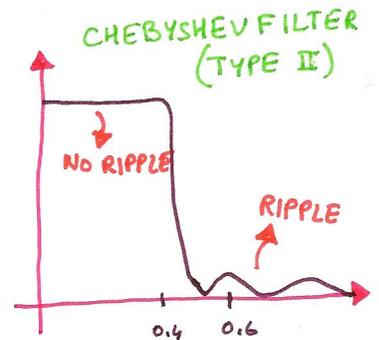
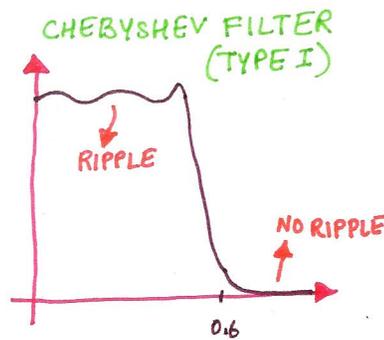


TENTATIVE PROBLEMS.

Chebyshev Filters:

Chebyshev filters have steeper roll-off than Butterworth filters but at the cost of having more passband ripple (type I) or more stop band ripple (type II) than the Butterworth filters.

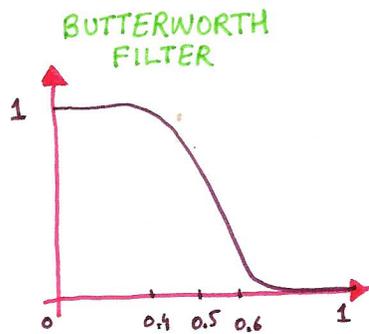

PROBLEM 1:

Obtain the transfer function for an analog chebyshev high-pass filter, which satisfies the following specification:

Passband Edge Frequency = 3000 r/s
Stopband Edge Frequency = 1000 r/s
Passband Attenuation = 0.5 dB
Stopband Attenuation = 22 dB

Afterwards, build up the circuit realization of the filter ($n=3$).

ANSWER 1:

Since specifications for high-pass filter are given but we have the design Equations for designing a low-pass filter. We will convert the specification to match low pass filter.

Passband Edge Frequency = 1000 r/s
Stopband Edge Frequency = 3000 r/s
Passband Attenuation = 0.5 dB
Stopband Attenuation = 22 dB

← NEW SPECIFICATIONS

To make our calculations easier, we can reduce the passband and stopband Edge frequencies by some factor and later add these factors in the transfer function.

Ω_p	Passband Edge Frequency = 1 r/s
Ω_s	Stopband Edge Frequency = 3 r/s
R_p	Passband Attenuation = 0.5 dB
A_s	Stopband Attenuation = 22 dB

Parameters of Filter Design:

- R_p = Passband Ripple
- A_s = Stopband Attenuation
- Ω_p = Passband cut-off Frequency
- Ω_s = Stopband cut-off Frequency

LET THE DESIGNING BEGIN!

STAGE 1: FINDING PARAMETERS.

STEP 1:

$$\epsilon = \sqrt{10^{0.1(R_p)} - 1}$$

$$\epsilon = \sqrt{10^{(0.1 \times 0.5)} - 1} = 0.349$$

$$\epsilon = 0.349$$

STEP 2:

$$A = 10^{\left(\frac{A_s}{20}\right)}$$

$$A = 10^{\left(\frac{22}{20}\right)} = 12.6$$

$$A = 12.6$$

STEP 3:

$$\Omega_c = \Omega_p = 1 \text{ r/s}$$

$$\Omega_r = \frac{\Omega_s}{\Omega_c} = \frac{3}{1} = 3$$

$$\Omega_r = 3$$

STEP 4:

$$g = \sqrt{\frac{(A^2 - 1)}{\epsilon^2}}$$

$$g = \sqrt{\frac{(12.6)^2 - 1}{(0.349)^2}} = 35.989$$

$$g = 36.0$$

STEP 5:

$$N = \left\lceil \frac{\log_{10} [g + \sqrt{g^2 - 1}]}{\log_{10} [\Omega_r + \sqrt{\Omega_r^2 - 1}]} \right\rceil$$

⌈ ⌉ = take ceiling

$$N = \left\lceil \frac{\log_{10} [36 + \sqrt{36^2 - 1}]}{\log_{10} [3 + \sqrt{3^2 - 1}]} \right\rceil = \lceil 2.43 \rceil = 3$$

$$N = 3$$

STAGE 2: FINDING POLES & ZEROS.

STEP 1:

$$k = 0, 1, \dots, N-1$$

$$k = 0, 1, 2$$

$$k = 0, 1, 2$$

$$p_k = \sigma_k + j\Omega_k$$

$$p_0 = \sigma_0 + j\Omega_0$$

$$p_1 = \sigma_1 + j\Omega_1$$

$$p_2 = \sigma_2 + j\Omega_2$$

Three poles. So two of them should have imaginary part and should be conjugates of each others. One pole would be real.

STEP 2:

$$\alpha = \frac{1}{\epsilon} + \sqrt{1 + \frac{1}{\epsilon^2}}$$

$$\alpha = \frac{1}{0.349} + \sqrt{1 + \frac{1}{(0.349)^2}} = 5.90$$

$$\alpha = 5.90$$

STEP 3:

$$a = \frac{1}{2} \left(\sqrt[N]{\alpha} - \sqrt[N]{\frac{1}{\alpha}} \right)$$

$$b = \frac{1}{2} \left(\sqrt[N]{\alpha} + \sqrt[N]{\frac{1}{\alpha}} \right)$$

$$a = \frac{1}{2} \left(\sqrt[3]{5.90} - \sqrt[3]{\frac{1}{5.90}} \right)$$

$$b = \frac{1}{2} \left(\sqrt[3]{5.90} + \sqrt[3]{\frac{1}{5.90}} \right)$$

$$a = 0.627$$

$$b = 1.180$$

$$a = 0.627$$

$$b = 1.180$$

STEP 4:

For p_0 :

$$\sigma_0 = (a \Omega_c) \cos \left(\frac{\pi}{2} + \frac{(2K+1)\pi}{2N} \right)$$

$$\sigma_0 = (0.627 \times 1) \cos \left(\frac{\pi}{2} + \frac{\pi}{6} \right) = -0.3135$$

$$\Omega_0 = (b \Omega_c) \cos \sin \left(\frac{\pi}{2} + \frac{(2K+1)\pi}{2N} \right)$$

$$\Omega_0 = (1.180 \times 1) \sin \left(\frac{\pi}{2} + \frac{\pi}{6} \right) = 1.02$$

$$p_0 = -0.314 + 1.02j \rightarrow \text{Conjugate of } p_a$$

For p_1 :

$$\sigma_1 = (a \Omega_c) \cos \left(\frac{\pi}{2} + \frac{(2K+1)\pi}{2N} \right)$$

$$\sigma_1 = (0.627 \times 1) \cos \left(\frac{\pi}{2} + \frac{3\pi}{6} \right) = -0.627$$

$$\Omega_1 = (b \Omega_c) \sin \left(\frac{\pi}{2} + \frac{(2K+1)\pi}{2N} \right)$$

$$\Omega_1 = (1.180 \times 1) \sin \left(\frac{\pi}{2} + \frac{3\pi}{6} \right) = 0$$

$$p_1 = -0.627 + 0j \rightarrow \text{Entirely Real}$$

For p_2 :

$$\sigma_2 = (a \Omega_c) \cos \left(\frac{\pi}{2} + \frac{(2K+1)\pi}{2N} \right)$$

$$\sigma_2 = (0.627 \times 1) \cos \left(\frac{\pi}{2} + \frac{5\pi}{6} \right) = -0.3135$$

$$\Omega_2 = (b \Omega_c) \sin \left(\frac{\pi}{2} + \frac{(2K+1)\pi}{2N} \right)$$

$$\Omega_2 = (1.180 \times 1) \sin \left(\frac{\pi}{2} + \frac{5\pi}{6} \right) = -1.02$$

$$p_2 = -0.3135 - 1.02j \rightarrow \text{Conjugate of } p_0$$

STAGE 3: BUILDING UP THE TRANSFER FUNCTION

STEP 1:

Now the system function is:

$$H_a(s) = \frac{K}{\prod_k (s + p_k)}$$

Assume $K=1$ unless otherwise told

$$H_{LP}(s) = \frac{1}{(s + 0.314 - 1.02j)(s + 0.627)(s + 0.314 + 1.02j)}$$

LOW PASS
TRANSFER
FUNCTION

SIMPLIFYING:

$$H_{LP}(s) = \frac{1}{(s^2 + 0.941s - 1.02sj - 0.64j + 0.197)(s + 0.314 + 1.02j)}$$

$$H_{LP}(s) = \frac{1}{s^3 + 1.255s^2 + 1.533s + 0.714}$$

WOLFRAM
CHECKED

STEP 2:

low pass to high pass transformation.

$$s = j\omega \xrightarrow{\text{REPLACE}} \frac{\omega_0}{j\omega} \quad \omega_0 = 3000 \text{ r/s}$$

$$H_{HP}(s) = \frac{1}{\left(\frac{3000}{j\omega}\right)^3 + 1.255 \left(\frac{3000}{j\omega}\right)^2 + 1.533 \left(\frac{3000}{j\omega}\right) + 0.714} \times \frac{(j\omega)^3}{(j\omega)^3}$$

$$H_{HP}(s) = \frac{(j\omega)^3}{2.7 \times 10^{10} + 1.13 \times 10^7 j\omega + 4599(j\omega)^2 + 0.714(j\omega)^3}$$

STAGE 4: PASSIVE CIRCUIT REALIZATION.

FROM THE TABLE ON SLIDE 70.

$$\text{Order} = n = 3$$

$$C_1 = 2.216$$

$$L_2 = 1.088$$

$$C_3 = 2.216$$




WARNING:

THE QUESTION ASKS FOR 0.5dB OF RIPPLE BUT IN THE TABLE IN SLIDES, THE VALUES ARE GIVEN FOR 1dB RIPPLE. IN EXAM BE CAREFUL.

STEP 1:

NORMALIZED HIGH PASS FILTER.

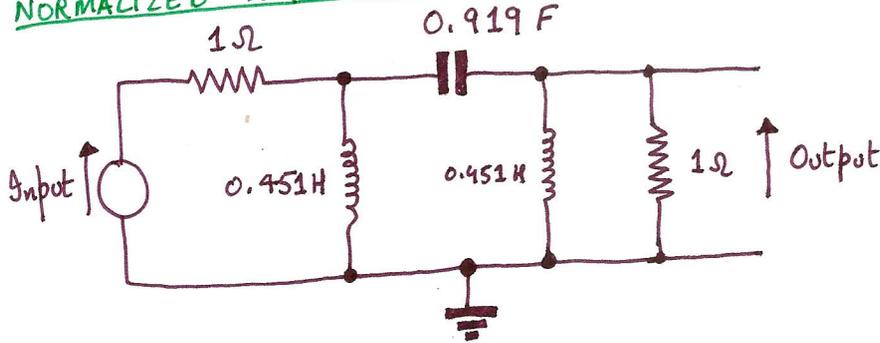

$$K = 1$$


STEP 2:

CONSIDER SOME K. (SCALE IMPEDANCES)

If we choose some high value of K , then the values of capacitors and inductors reach the acceptable level.

$$K = 1000 \rightarrow \text{JUST RANDOMLY CHOSEN}$$

Now the circuit becomes :-

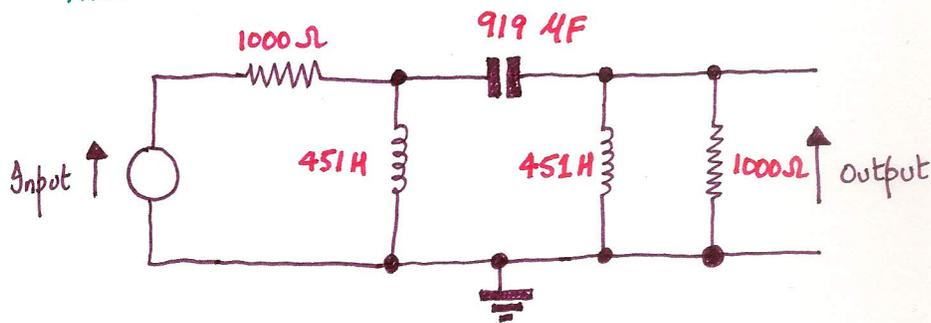


- MULTIPLY RESISTORS & INDUCTORS VALUES BY K
- DIVIDE CAPACITOR VALUES BY K

STEP 3:

SCALE FREQUENCY.

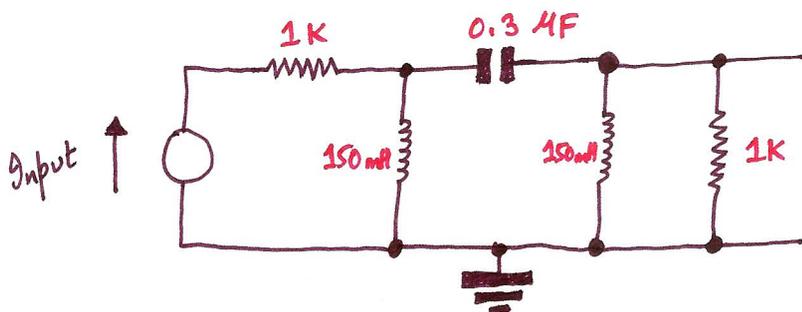Now we need to change the frequency at which our circuit operates to the one required in the question



- DIVIDE CAPACITOR & INDUCTOR VALUES BY $\omega_c \cdot \Omega_p$

STAGE 5: ACTIVE CIRCUIT REALIZATION.

STEP ①:

Divide the transfer function into first order and second order transfer function.

$$H_{HP}(s) = \frac{(j\omega)^2}{(s^2 + 1656s + 7.9 \times 10^6)} + \frac{j\omega}{(0.714s + 3416.7)}$$

This is a second order Equation which corresponds to Sallen-Key High-Pass Filter.

This is a first order high pass filter.

FOR SALLEN-KEY:

$$H_{HP}(s) = \frac{1.27 \times 10^7 (j\omega)^2}{1.27 \times 10^7 s^2 + 2.096 \times 10^{-4} s + 1}$$

$$\therefore T_1 T_2 = 1.27 \times 10^7$$

$$2T_1 = 2.096 \times 10^{-4}$$

$$\therefore T_1 = 1.05 \times 10^{-4}$$

$$\therefore T_2 = \frac{1.27 \times 10^7}{1.05 \times 10^{-4}} = 1.21 \times 10^{11}$$


$$C_1 = C_2$$

$$\text{let } C_1 = C_2 = 4 \text{ F}$$

then

$$R_2 = 3.025 \times 10^{10} \Omega$$


$$R_1 = 26 \mu\Omega$$

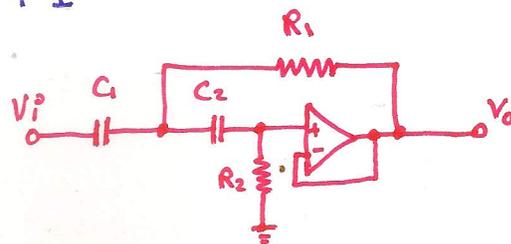

FOR FIRST ORDER HP:

$$H_{hp}(s) = \frac{1.4 s}{s + 4785}$$

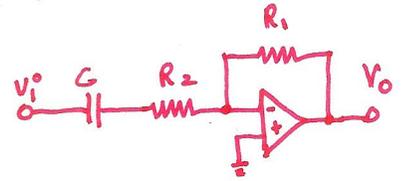$\xrightarrow{H_0}$
 $\xrightarrow{\omega_0}$




$$\omega_0 = \frac{1}{R_2 C} \quad H_0 = -\frac{R_1}{R_2} \quad |H_0| = \frac{R_1}{R_2}$$

$$1.4 = \frac{R_1}{R_2} \quad \text{if } R_2 = 1 \Omega \text{ then } R_1 = 1.4 \Omega$$

$$C = \frac{1}{R_2 \omega_0} = \frac{1}{1 \times 4785} = 208 \mu\text{F}$$

finally

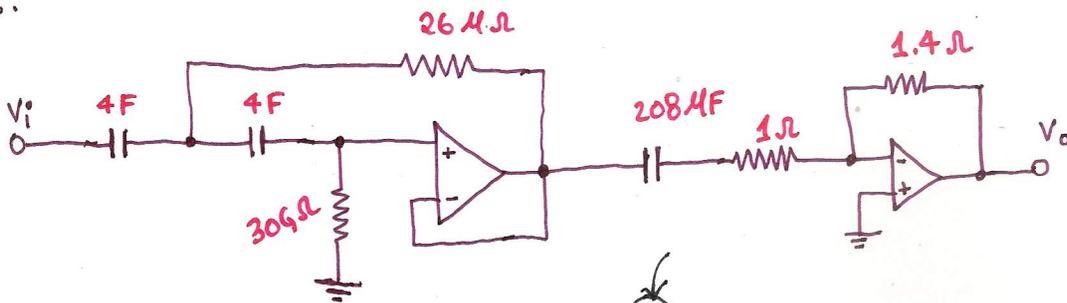

YALLA ENJOY ! 