

Electronic Devices and Circuits



Muhammad Obaidullah

Bilal Arshad Tarar

Introduction



Problem




- ✎ Design a Wien bridge oscillator to provide 18 KHz frequency.
- ✎ Use MULTSIM to simulate your oscillator.
- ✎ Modify oscillator for amplitude stabilization.
- ✎ Implement you design on PCB and test your circuit.


Designing the Circuit



Oscillators

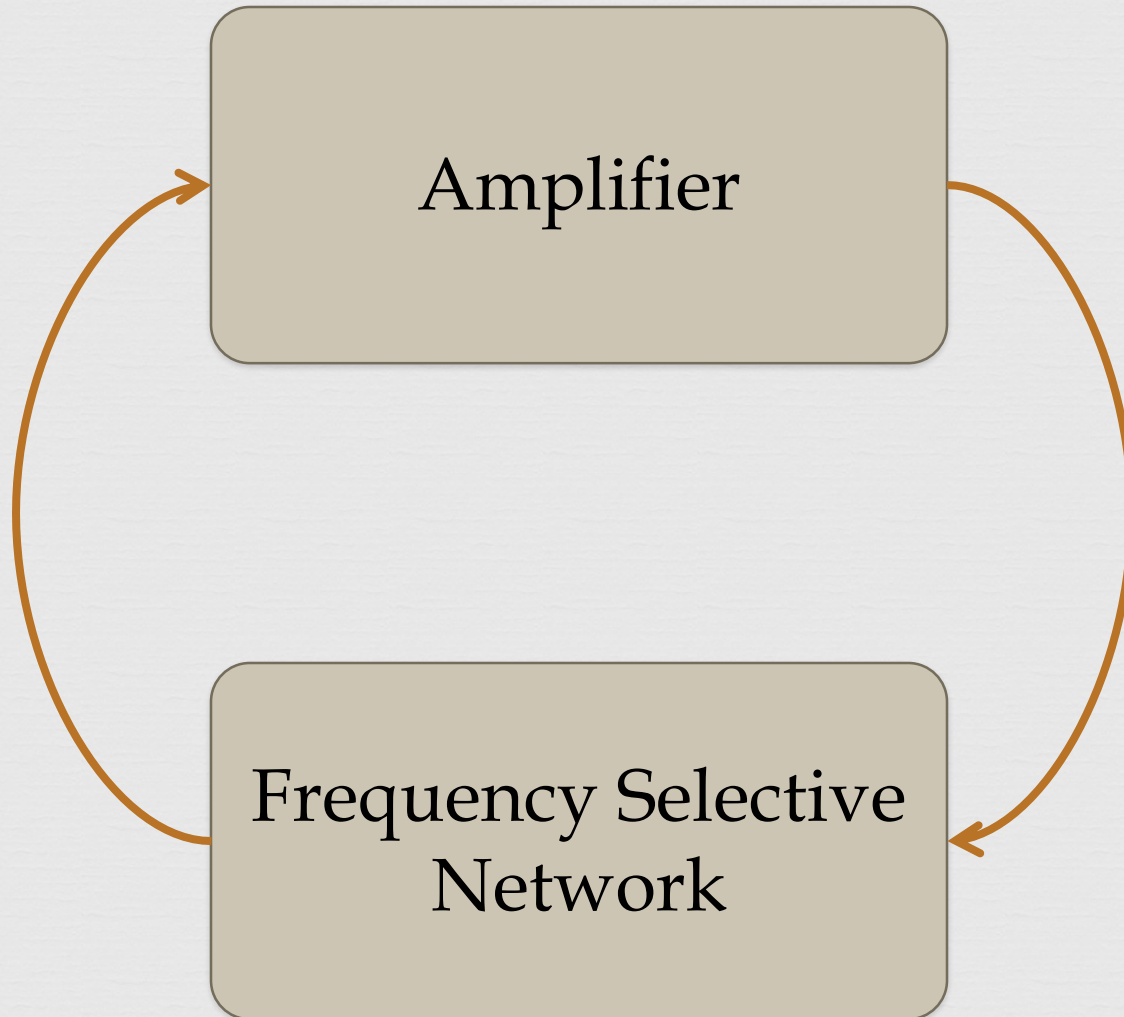

Oscillators

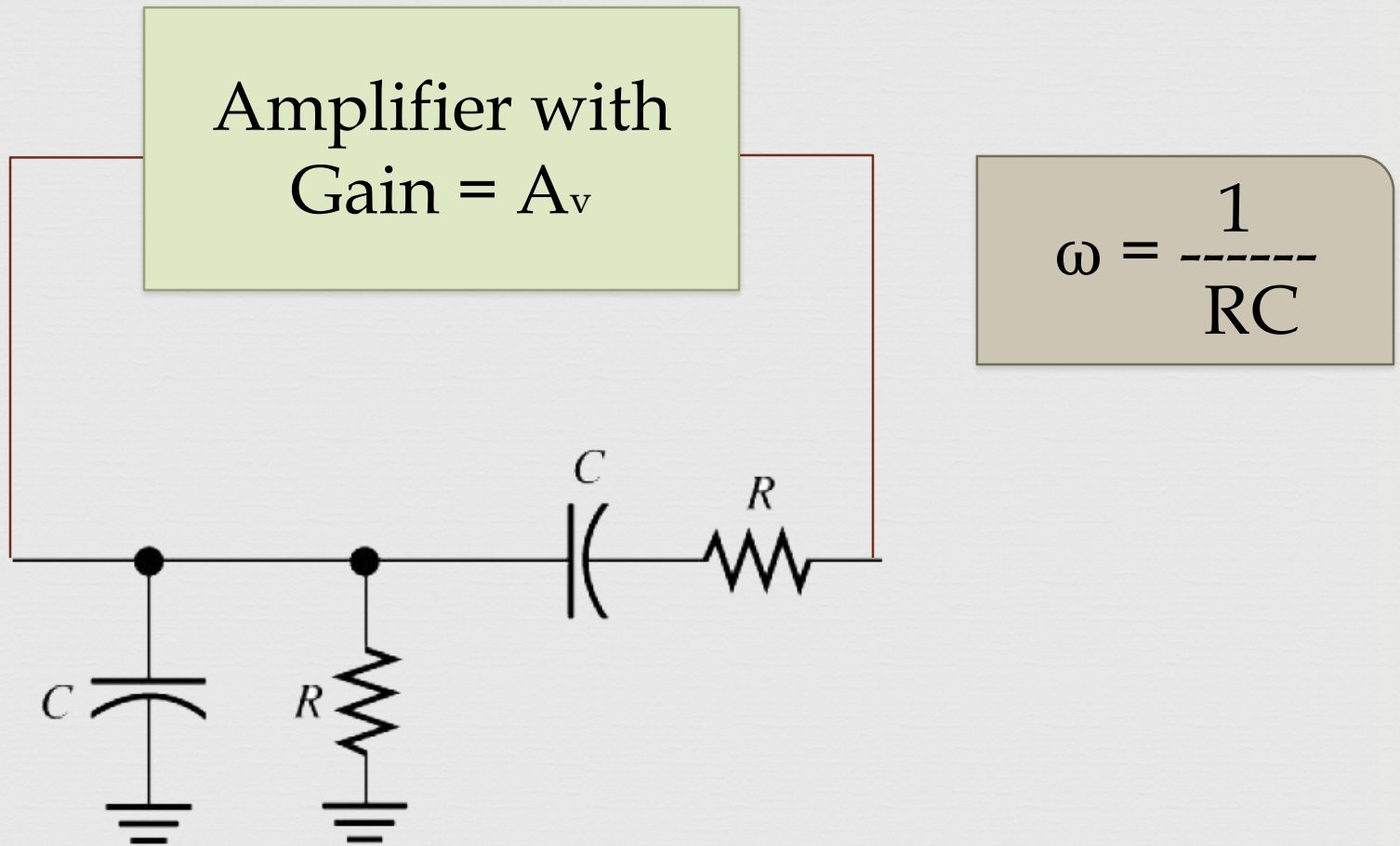

Finding Resistor Values

$$\omega = \frac{1}{RC}$$



$$f = \frac{1}{2\pi RC}$$




$$R = \frac{1}{2\pi fC}$$

$$R = \frac{1}{2\pi \times 1.5 \times 10^{-9} \times 18 \times 10^3}$$



$$R \approx 5.9 \text{ K}\Omega$$




$f = 18 \text{ KHz}$
 $C = 1.5 \text{ nF}$


Simulation



Setting the Environment

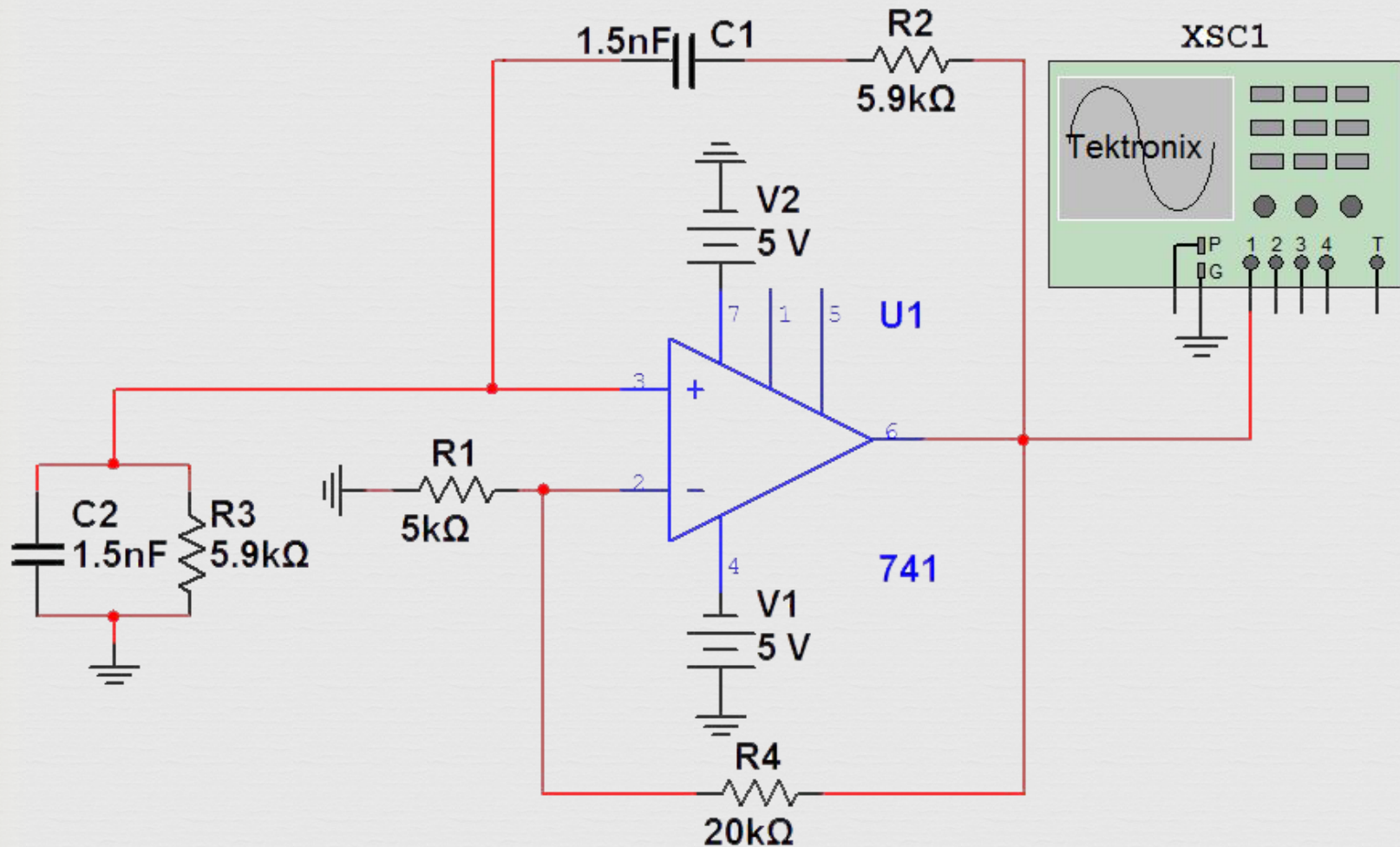


Finding the Right Gain

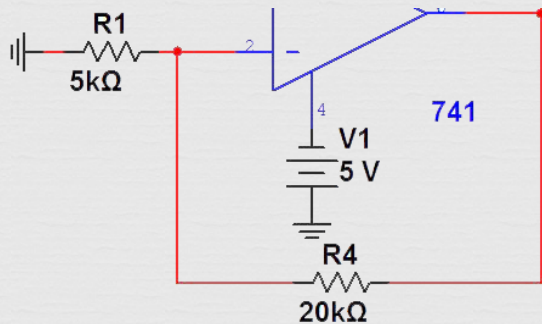

$$A_v = \frac{R4 + R1}{R1}$$

S.No.	R1	R4	Gain	Oscillation
1	5K	5K	2	No Oscillation
2	5K	10K	3	No Oscillation
3	5K	15K	4	Oscillation Present
4	5K	20K	5	Oscillation Present

Wien Bridge Oscillator

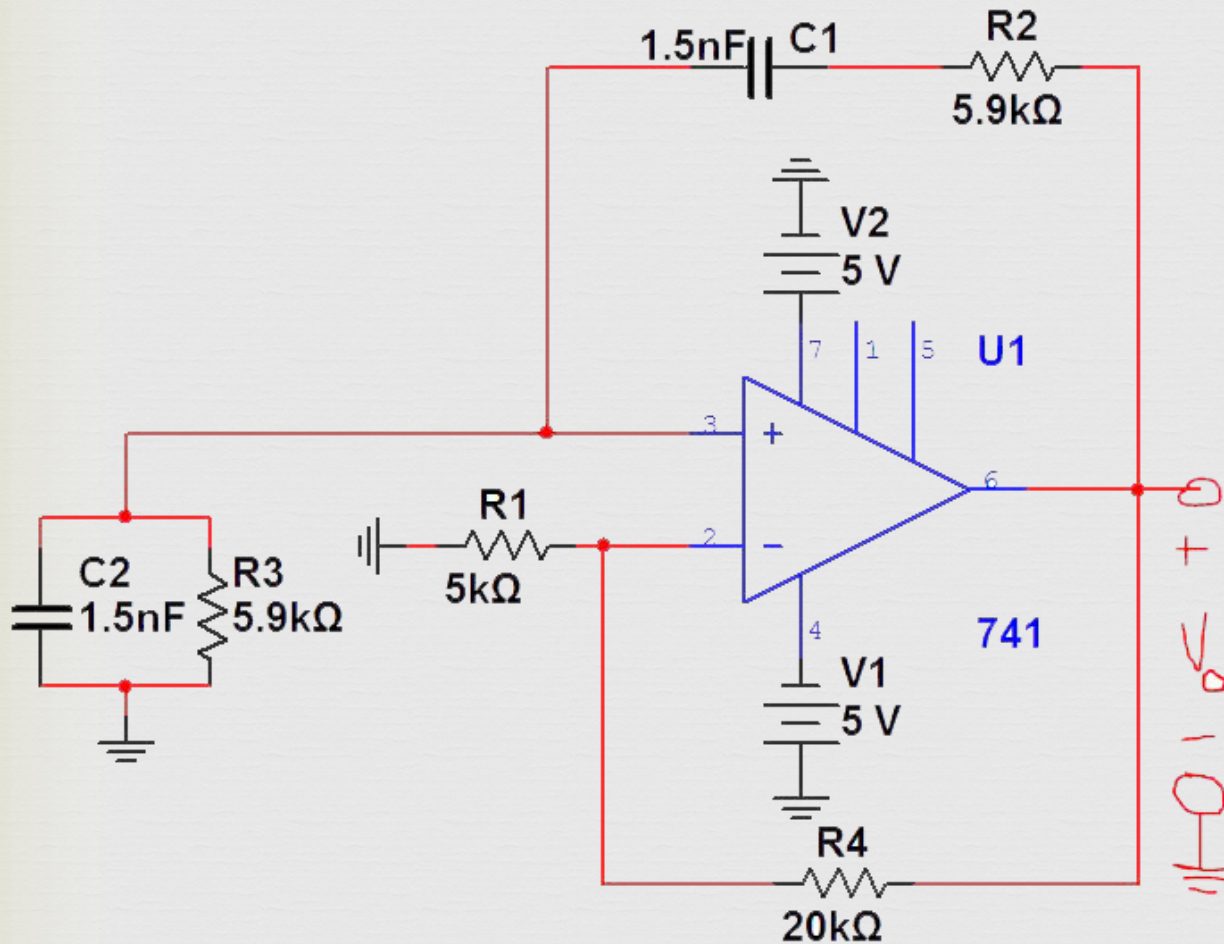

$$A_v = \frac{R4 + R1}{R1}$$




$$A_v = \frac{25}{5} = 5$$


Amplitude Stabilization




Amplitude Problem

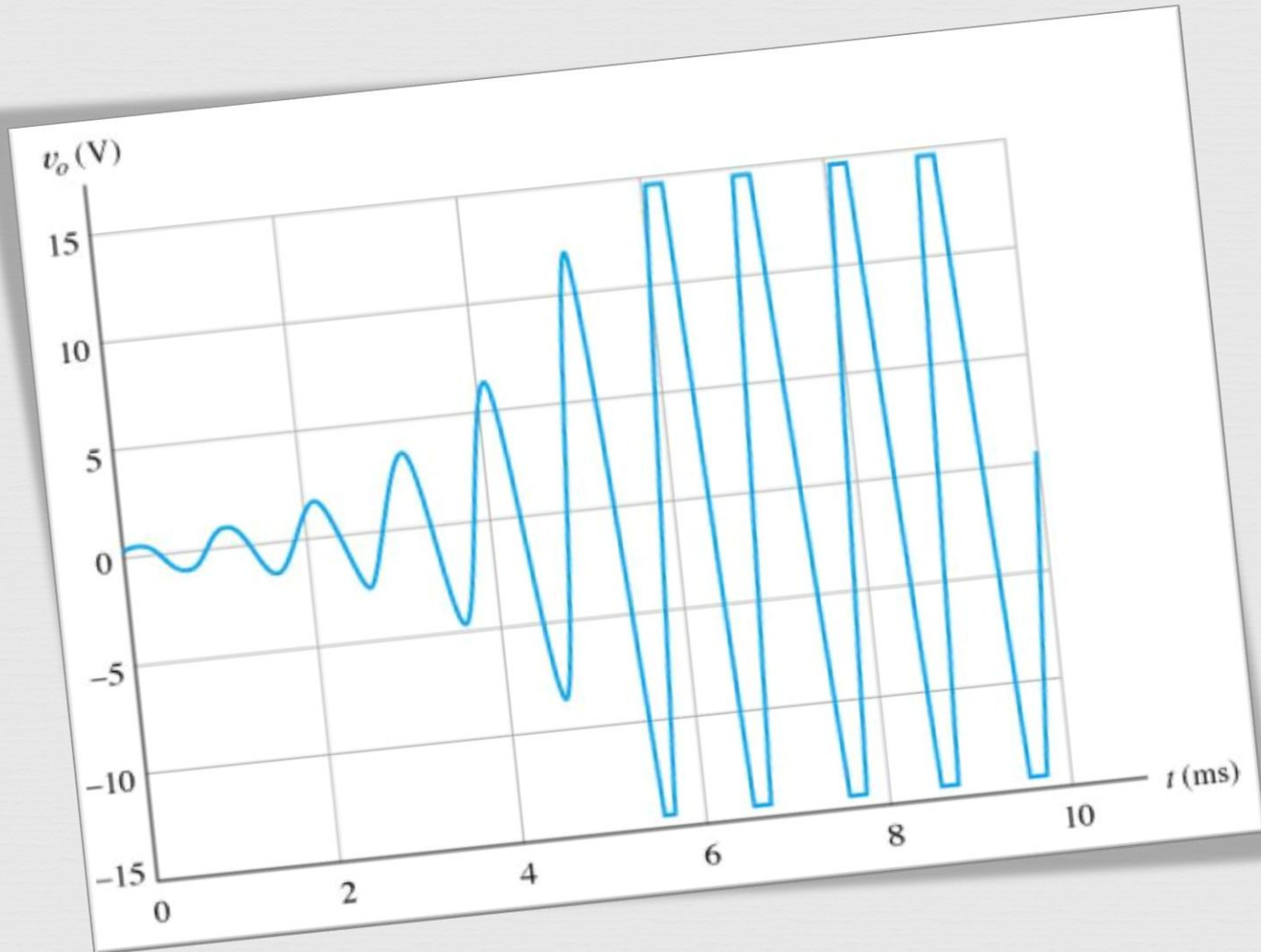


Possible Solution

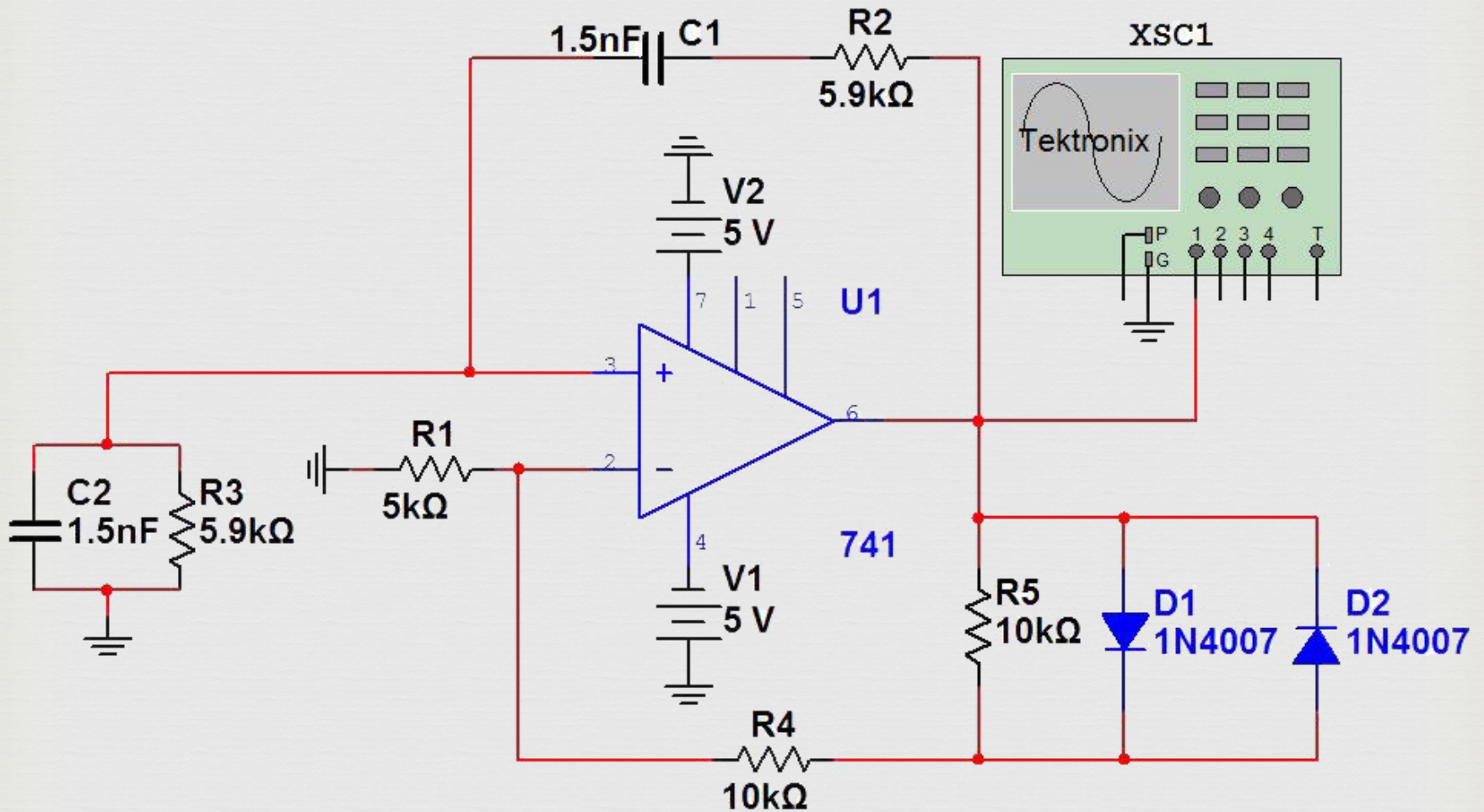


Possible Solution

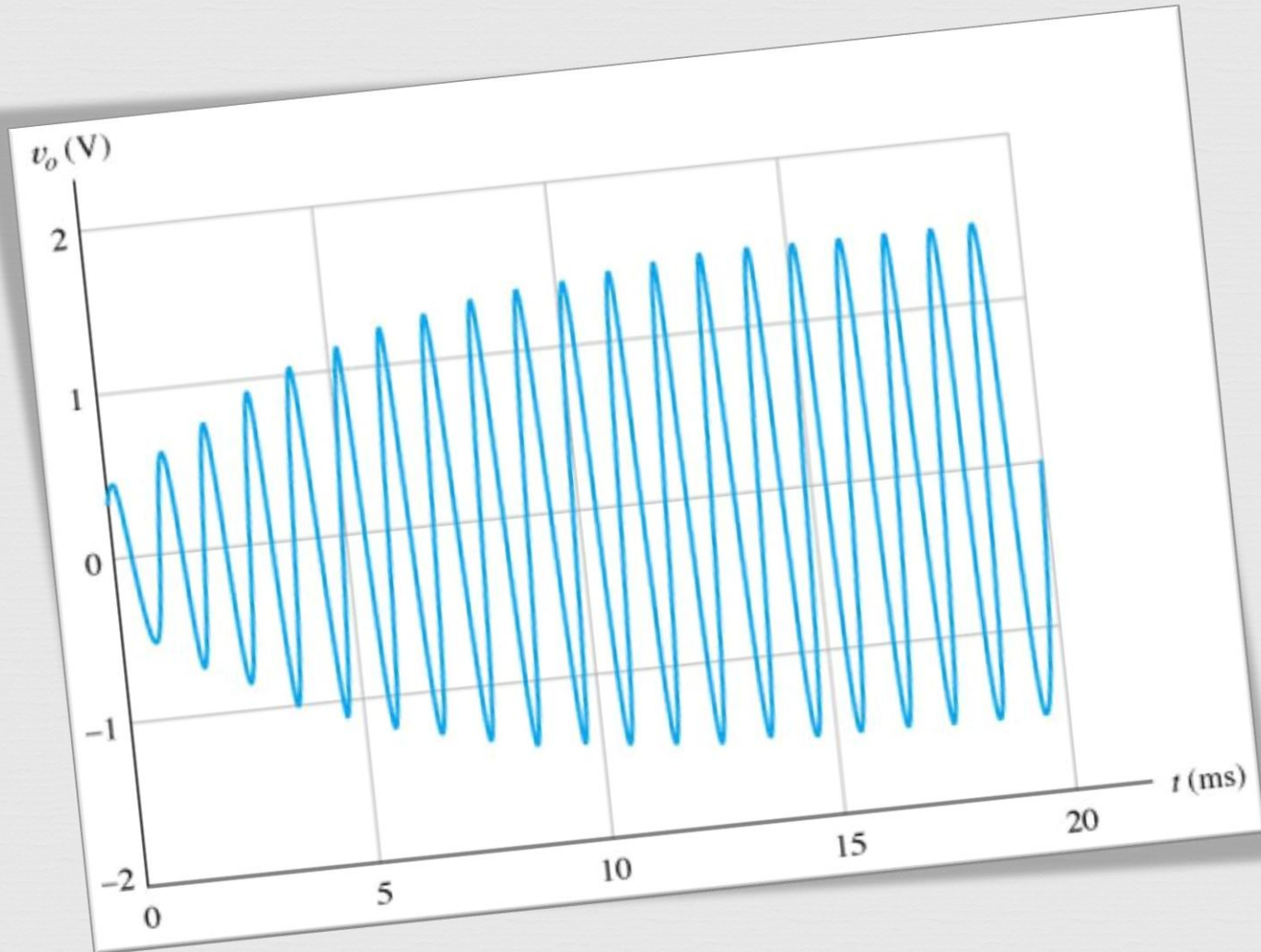

Solution Result

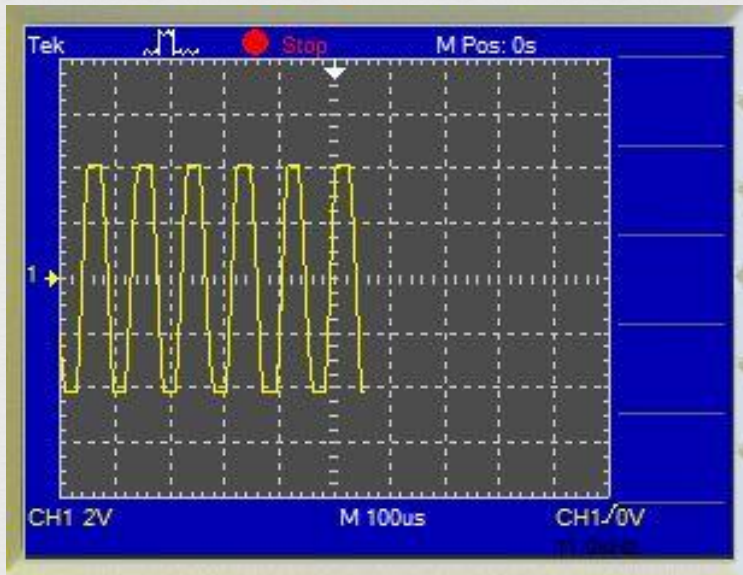

Before
(without diodes)


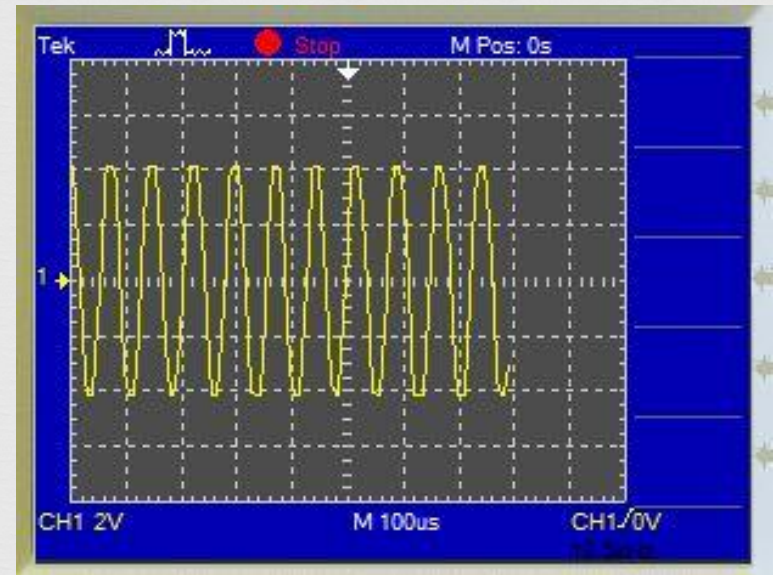


After
(with diodes)



Problems Faced



Frequency Problem

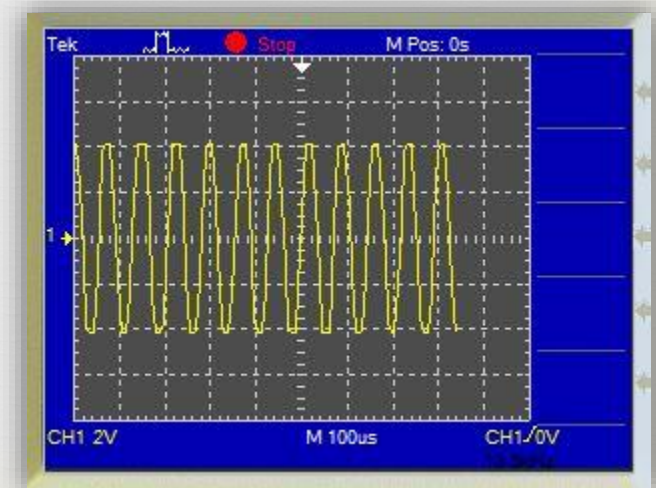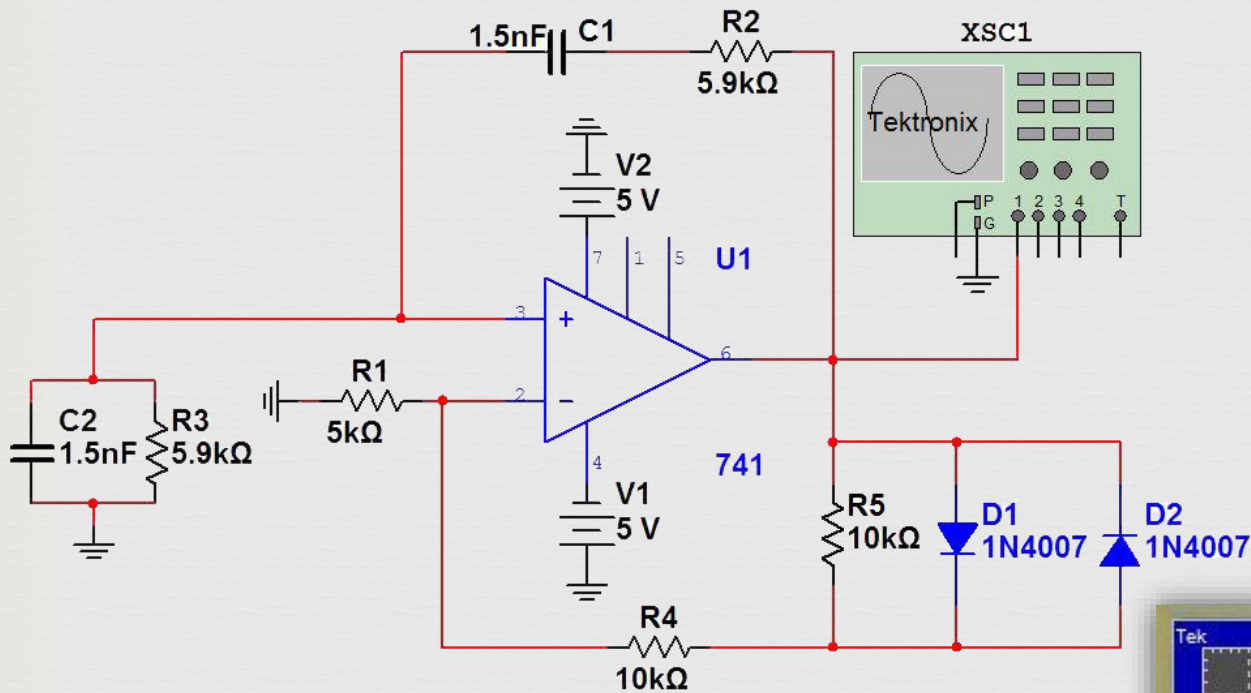

Frequency Solution

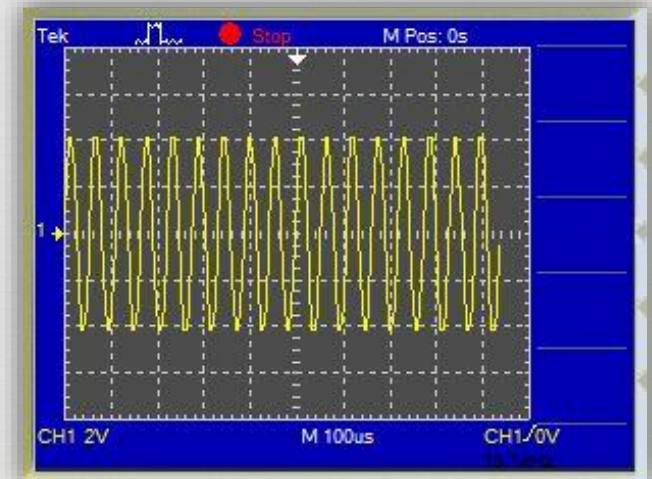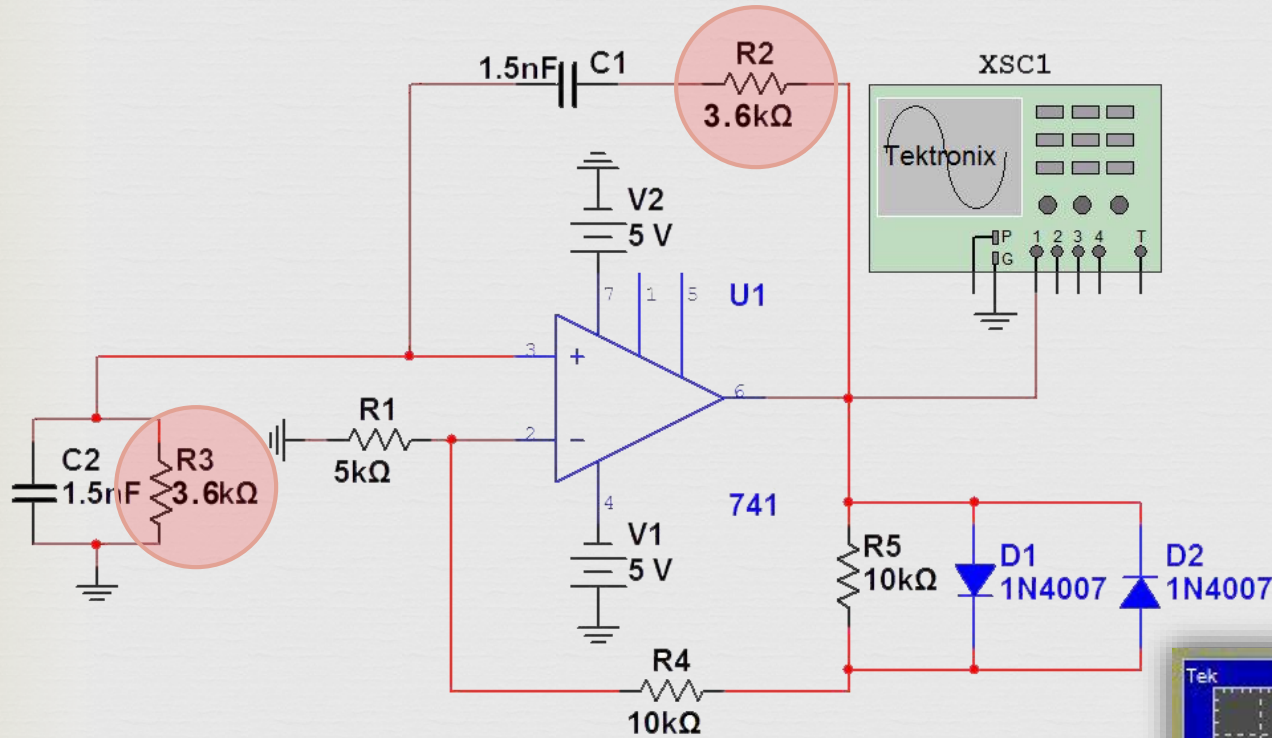


PCB and Testing




Final Circuit

3.6 K + (0 ↔ 1) K

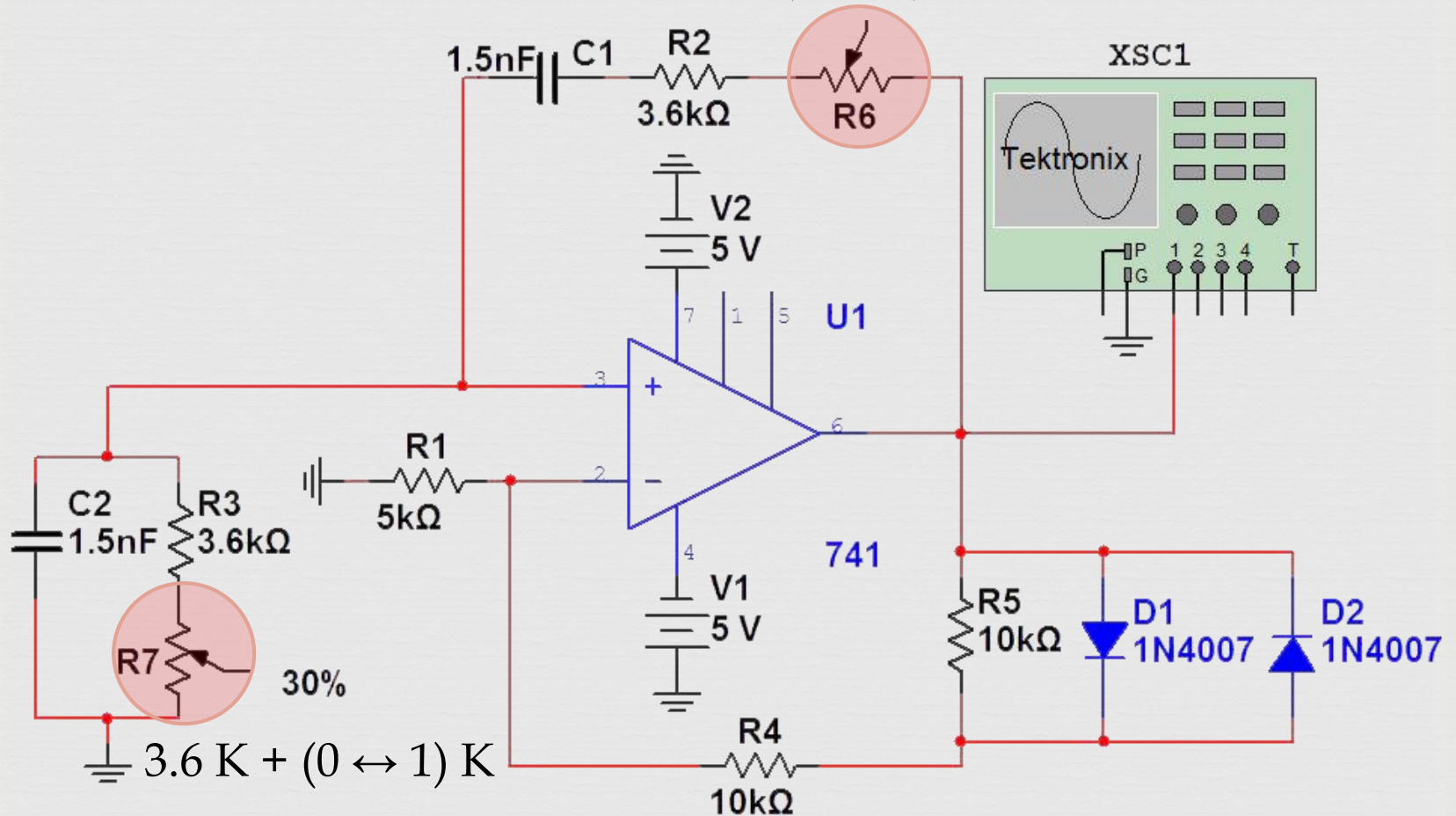


Final Circuit

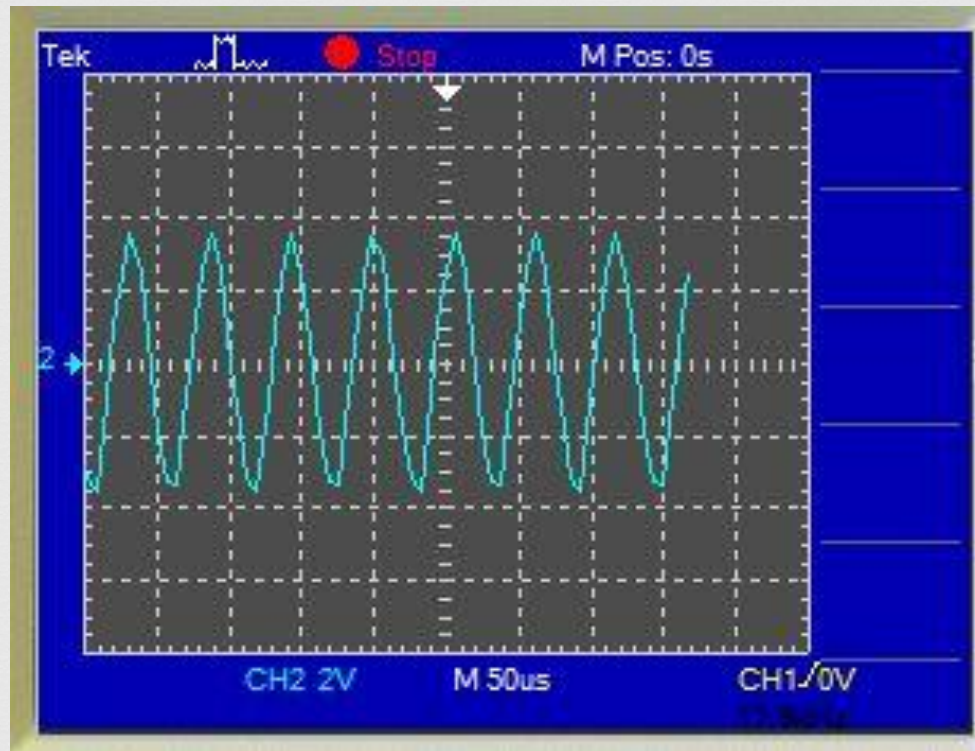



Oscilloscope Resulting Waveform

Going Further...

3.6 K + (0 ↔ 1) K

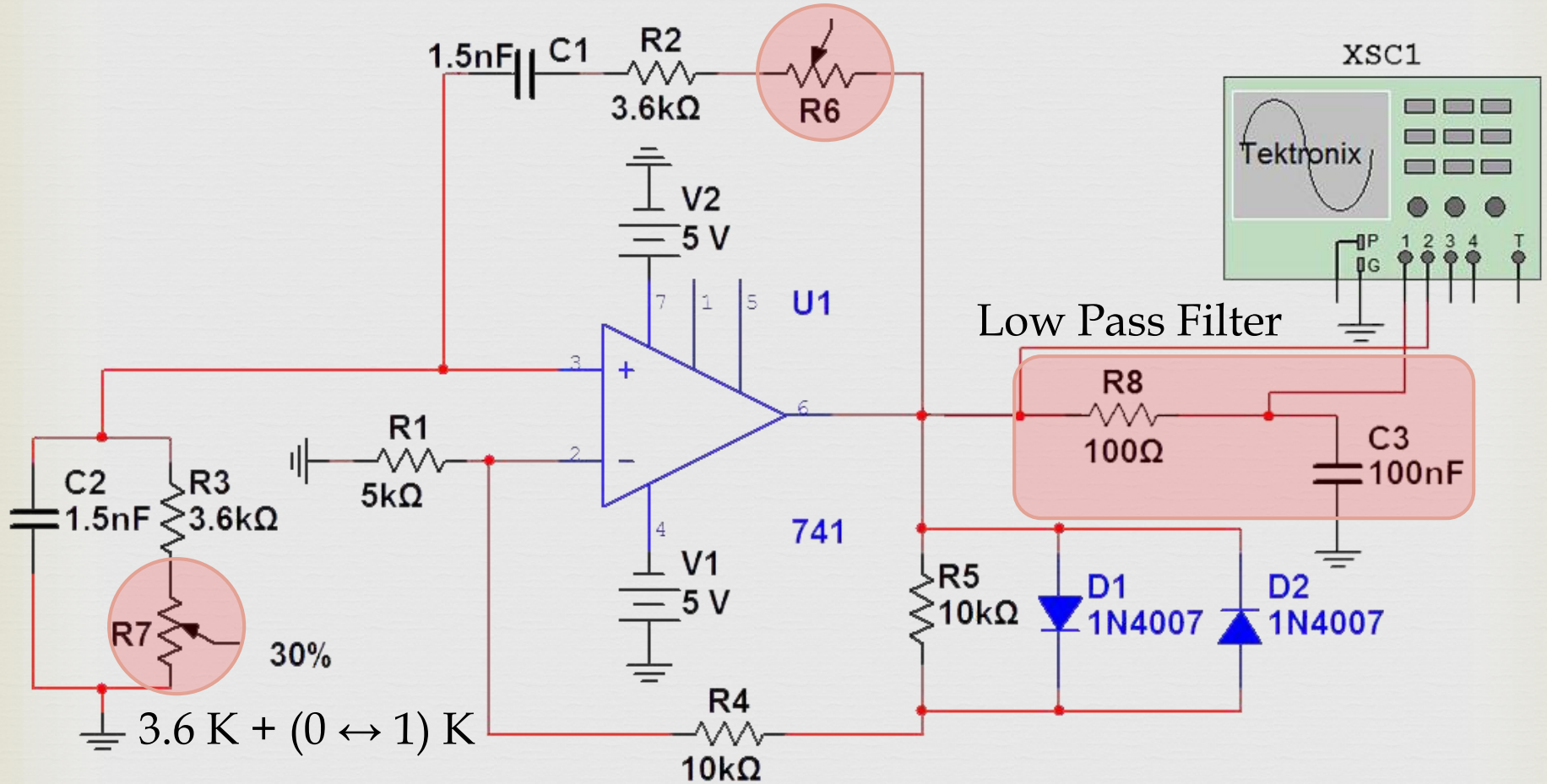


Going Further...

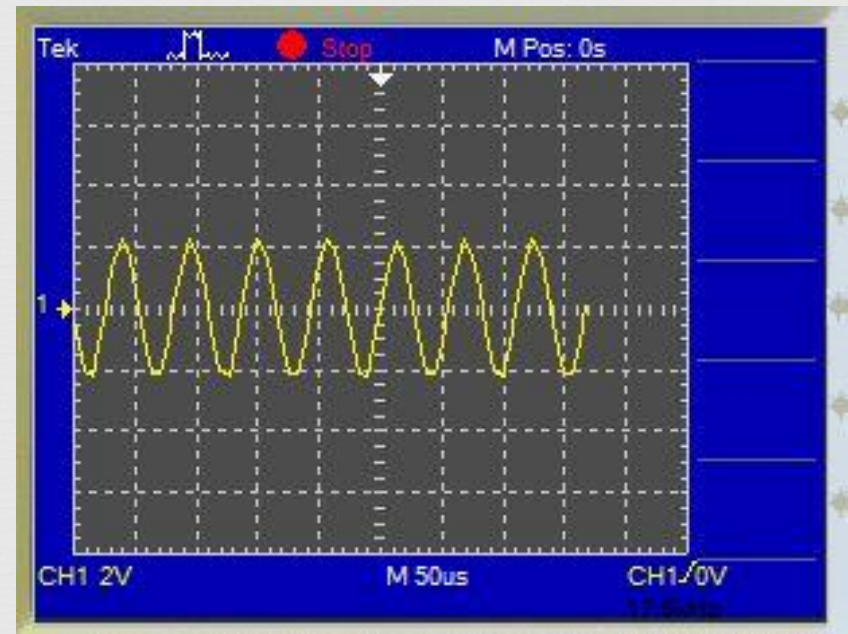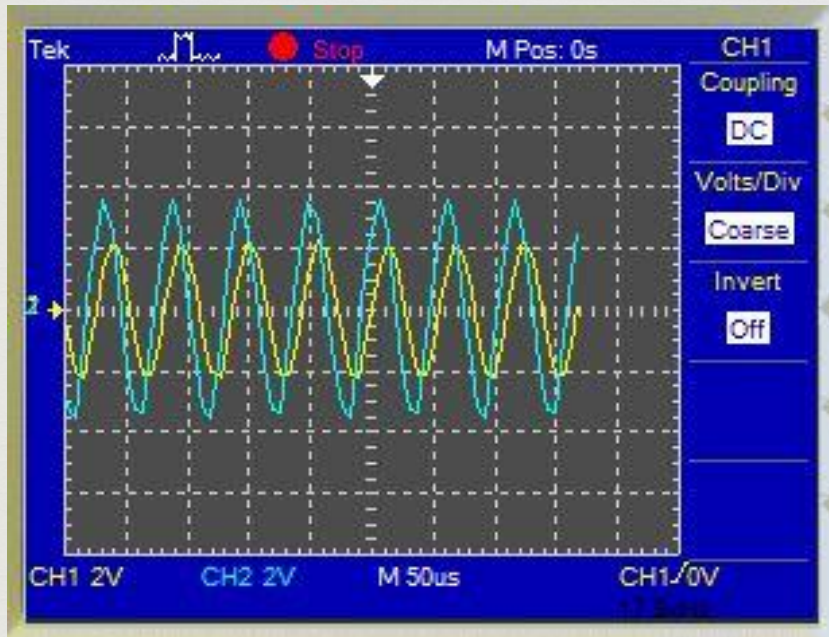

Blue – without low pass
Yellow – with low pass

PCB

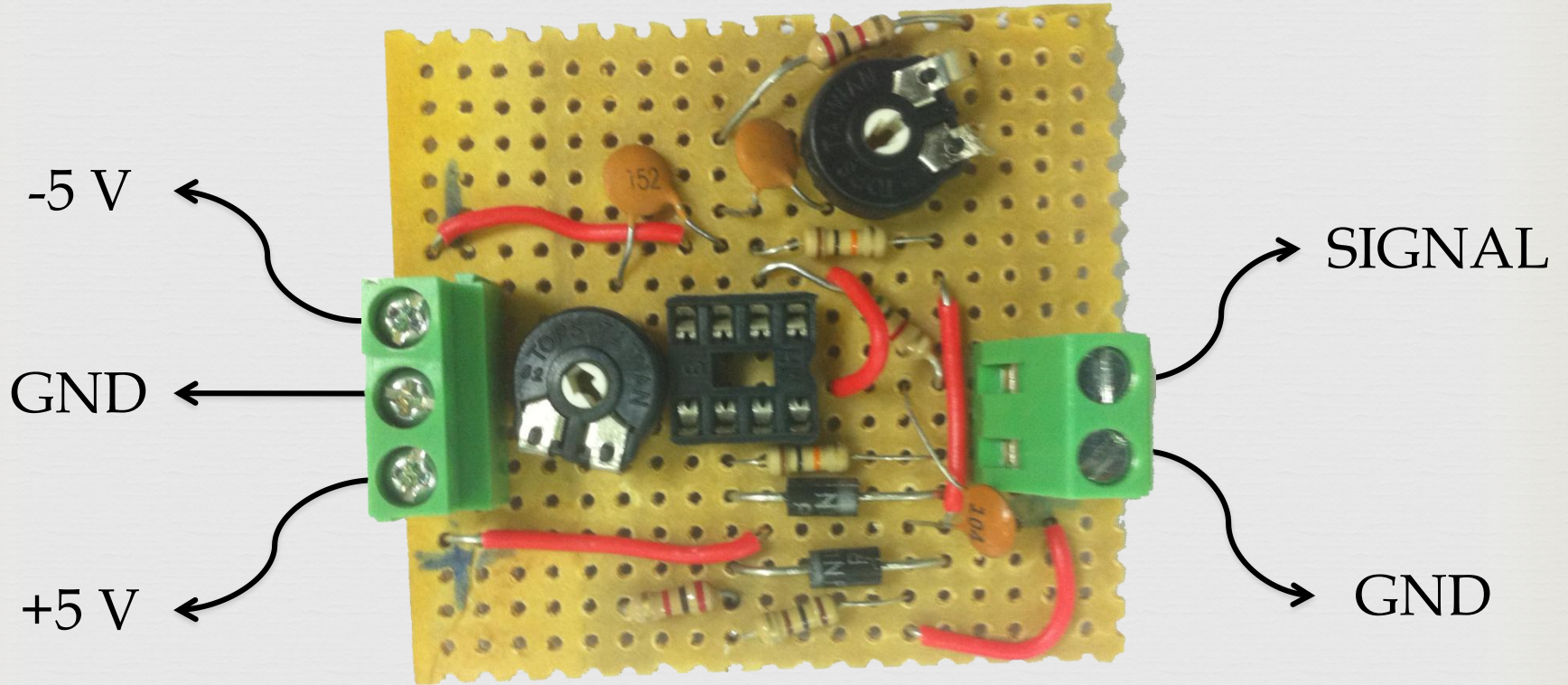

Video Demo

Conclusion



- ❧ Low pass filter can remove the harsh edges but it consumes power from the signal.
- ❧ RC circuit as a frequency filter is good but not accurate enough, for high accuracies we can use crystal oscillator.
- ❧ Wien bridge oscillator frequency depends on the input voltage.

- ✧ MULTISIM simulates close to real components and takes into account some probabilities.
- ✧ Amplifier gain should be above 3 for an oscillation to happen.
- ✧ Distortion happens if the input voltages ($-V$ and $+V$) are not equal.

Thank You

