

ENERGY CONVERSION FORMULA SHIT

1. DC MACHINES

✚ EFFICIENCY

✓ $Efficiency = \frac{P_{out}}{P_{in}} \times 100\%$

✓ $Efficiency = \frac{P_{in} - P_{loss}}{P_{in}} \times 100\%$

✚ ELECTRICAL OR COPPER LOSSES

✓ $Armature Loss = P_A = I_A^2 \times R_A$

✓ $Field Loss = P_F = I_F^2 \times R_F$

✚ BRUSH LOSSES

✓ $Brush Loss = P_{BD} = V_{BD} \times I_A$

✚ POWER FLOW

✓ $Electrical Power Converted = P_{conv} = E_A \times I_A$

✓ $Mechanical Power Converted = P_{conv} = \tau_{ind} \times \omega_m$

✚ TORQUE AND VOLTAGE

✓ $Internal Generated Voltage = E_A = K\phi\omega$

✓ $Induced Torque = \tau_{ind} = K\phi I_A$


✚ SEPERATELY EXCITED AND SHUNT DC MOTORS

✓ $Terminal Voltage = V_T = E_A + I_A R_A$

SPEED AND VOLTAGE

✓
$$\frac{\text{Speed with Load 1}}{\text{Speed with Load 2}} = \frac{n_1}{n_2} = \frac{E_{A1}}{E_{A2}}$$

DC SHUNT MOTOR EQUIVALENT CIRCUIT

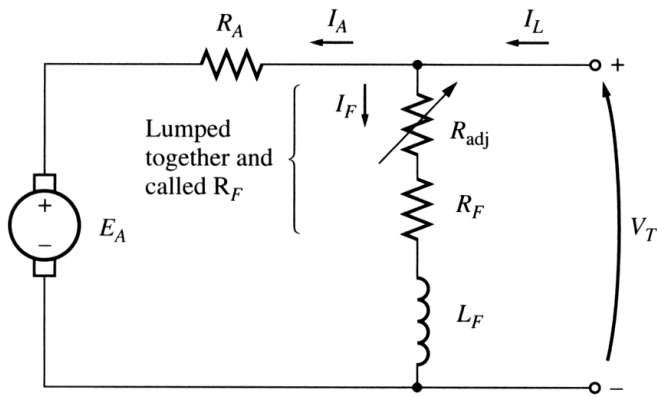


$$I_F = \frac{V_T}{R_F}$$

$$V_T = E_A + I_A R_A$$

$$I_L = I_A + I_F$$

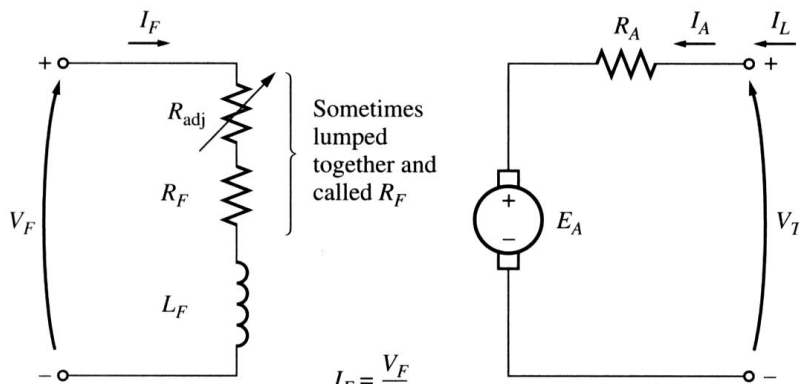DC SEPERATELY EXCITED MOTOR EQUIVALENT CIRCUIT




Sometimes lumped together and called R_F

$$I_F = \frac{V_F}{R_F}$$

$$V_T = E_A + I_A R_A$$

$$I_L = I_A$$

DC SERIES MOTOR EQUIVALENT CIRCUIT

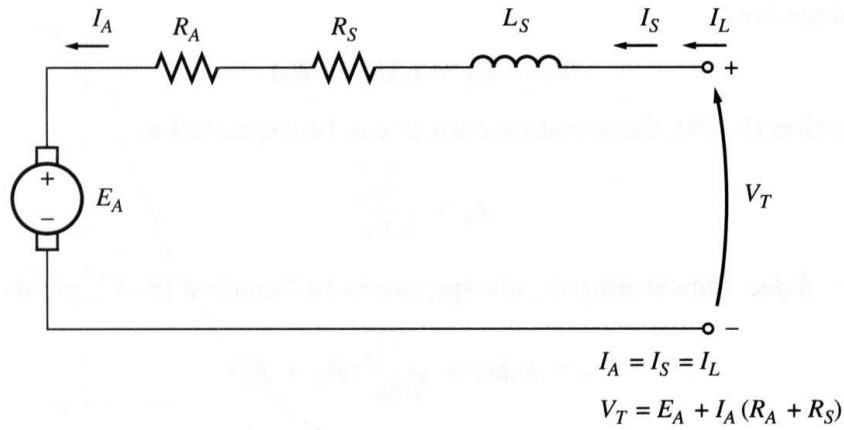


DC SERIES MOTOR TORQUE

✓ Induced Torque = $\tau_{ind} = KcI_A^2$

Where c is proportionality constant

DC COMPOUND MOTOR EQUIVALENT CIRCUIT

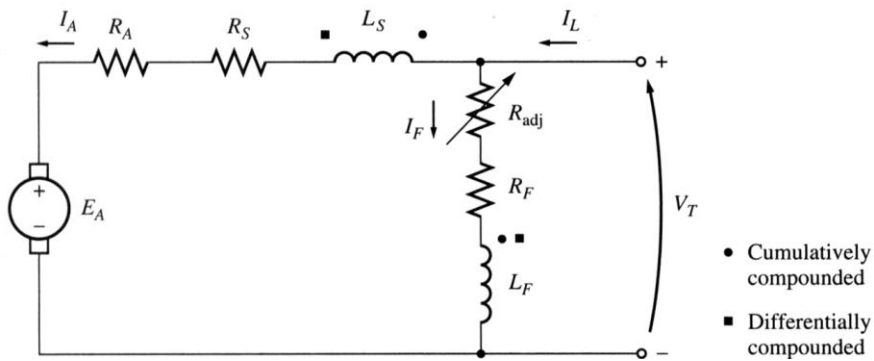

2. INDUCTION MOTORS

SPEED

$$\text{Slip Speed} = n_{slip} = n_{sync} - n_m$$

SLIP

$$\checkmark \text{ Slip} = s = \frac{n_{sync} - n_m}{n_{sync}}$$

FREQUENCY

$$\checkmark \text{ Rotor Frequency} = f_r = \frac{\text{No. of Stator Poles} \times \text{Slip Speed}}{120} = \frac{P \times n}{120}$$

$$\checkmark \text{ New Frequency} = f_r = s f_e$$

TORQUE AND POWER

$$\checkmark \text{ Torque of the Load} = \tau_{load} = \frac{P_{out}}{\omega_m}$$

$$\checkmark \omega_m = \frac{2\pi n_m}{60} \text{ rad/s}$$

HORSE POWER

$$\checkmark \text{ Horse Power} = hp = 746 \text{ Watts}$$

EQUIVALENT CIRCUIT

